

CO101

Principle of Computer Organization

Lecture 5: Multi-Cycle Processor


Liang Yanyan

澳門科技大學

Macau of University of Science and Technology

What's wrong with our CPI=1 processor?

Arithmetic & Logical

 

Load



← Critical Path →

Store




Branch




- Long Cycle Time.
- Real memory is not so nice as our idealized memory.
 - cannot always get the job done in one (short) cycle.

Reducing Cycle Time

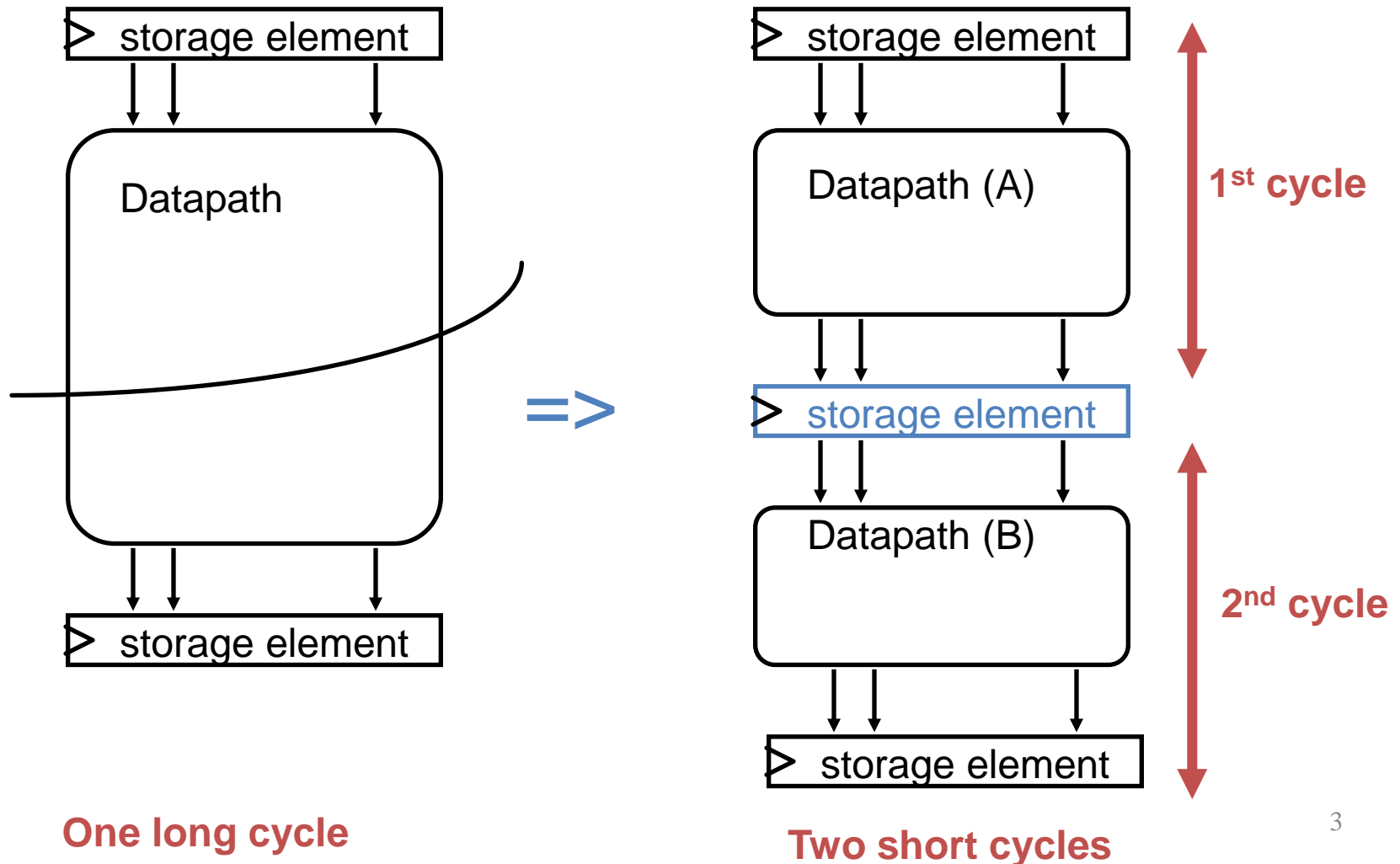- Cut combinational dependency graph and insert register.
- Do same work in two short cycles, rather than one long cycle.




Review: A Single Cycle Datapath

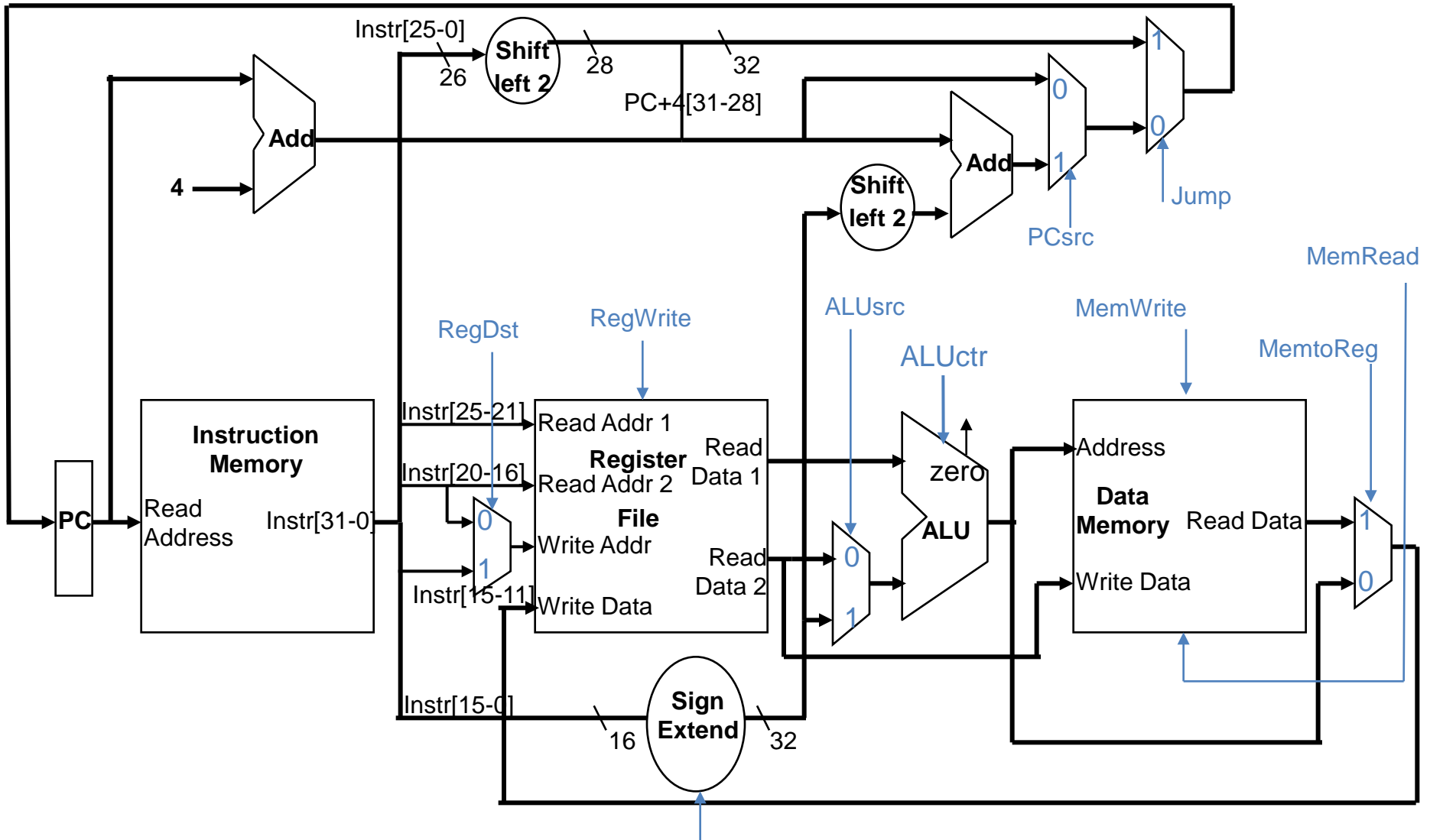


Partition the CPI=1 Datapath

- Add registers between partitions.

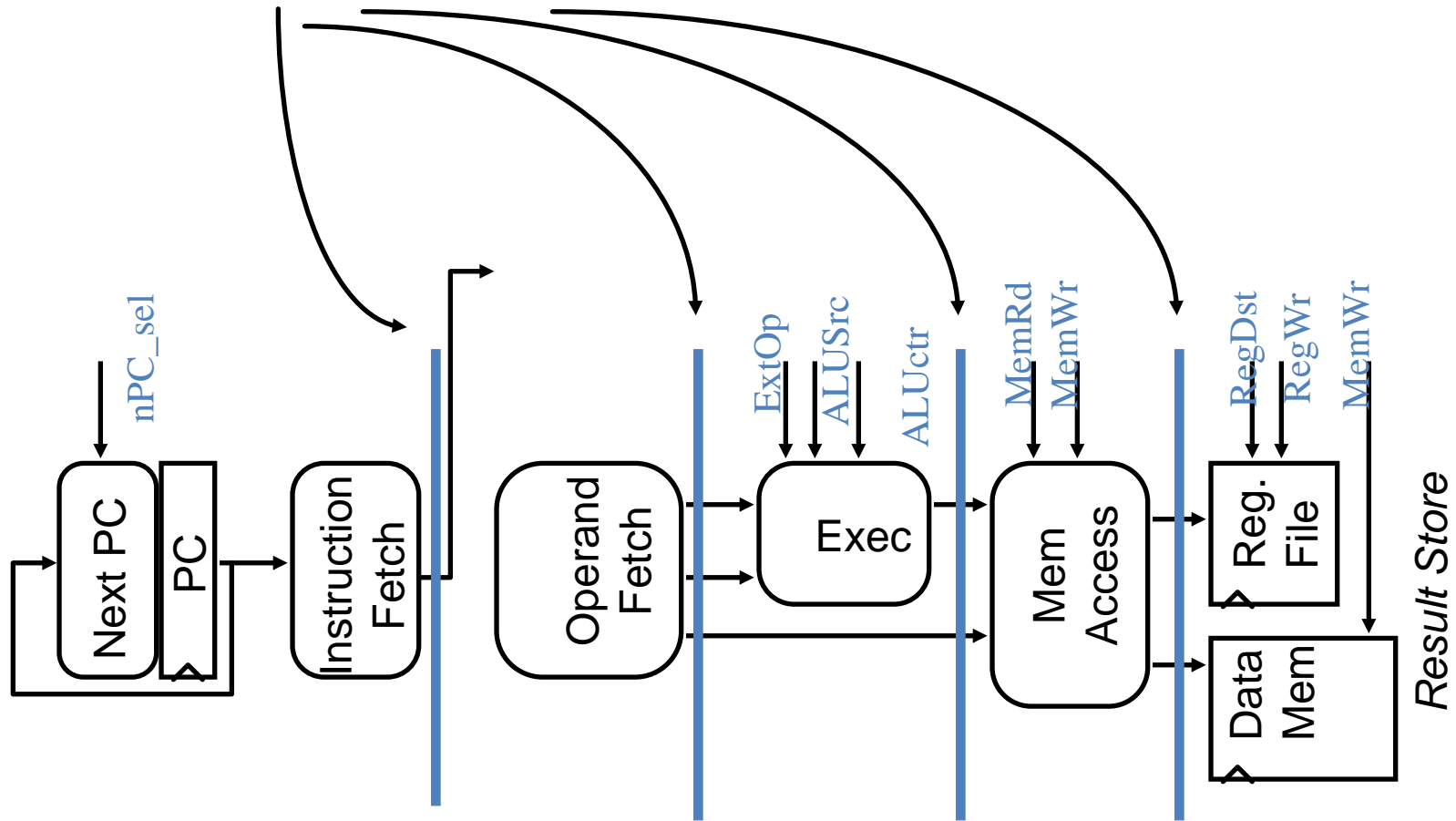

Partition the CPI=1 Datapath

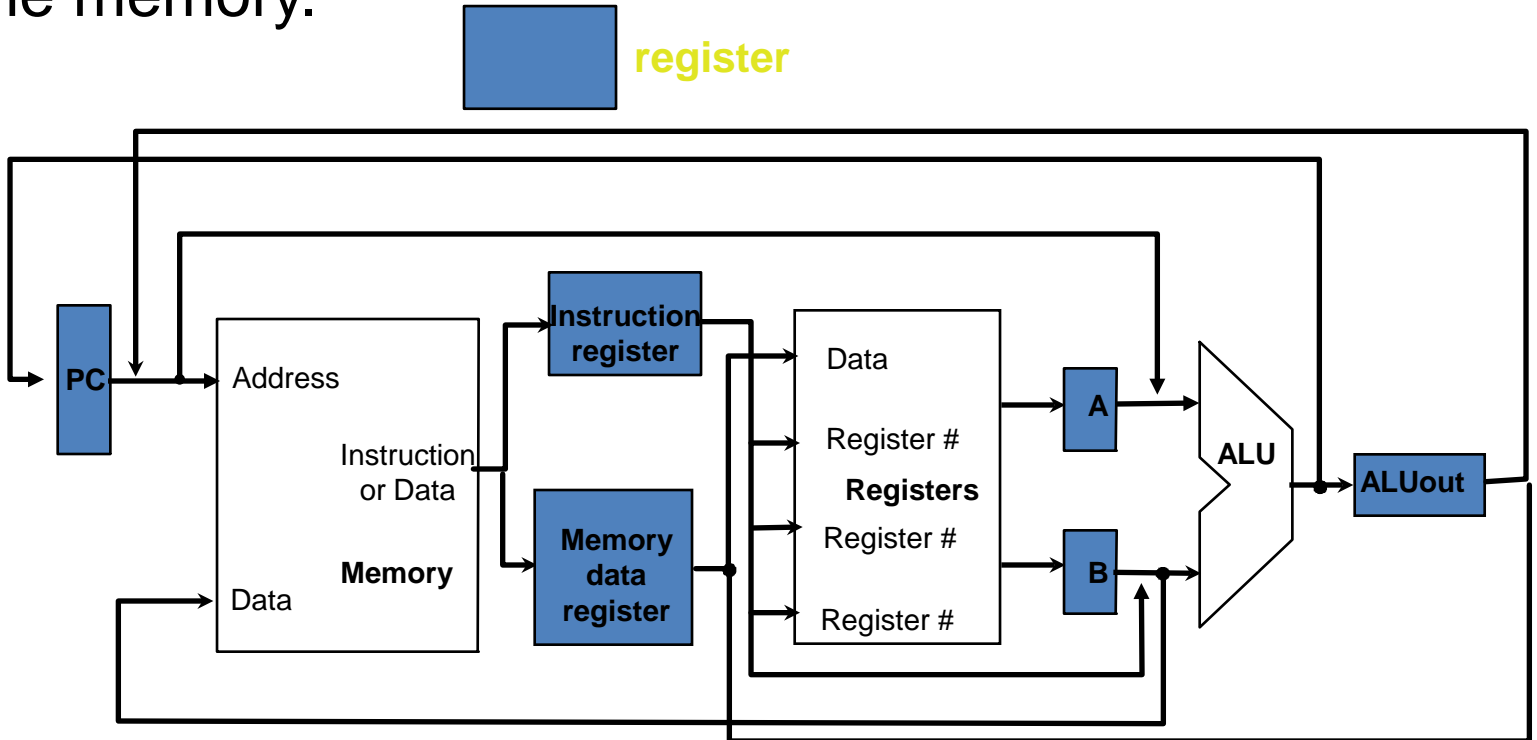- Instruction memory and data memory are combined into one memory.



load PC



Load
instruction
or data



Load data
from register
or store data
to register




Execute



Write
result

A more detailed view

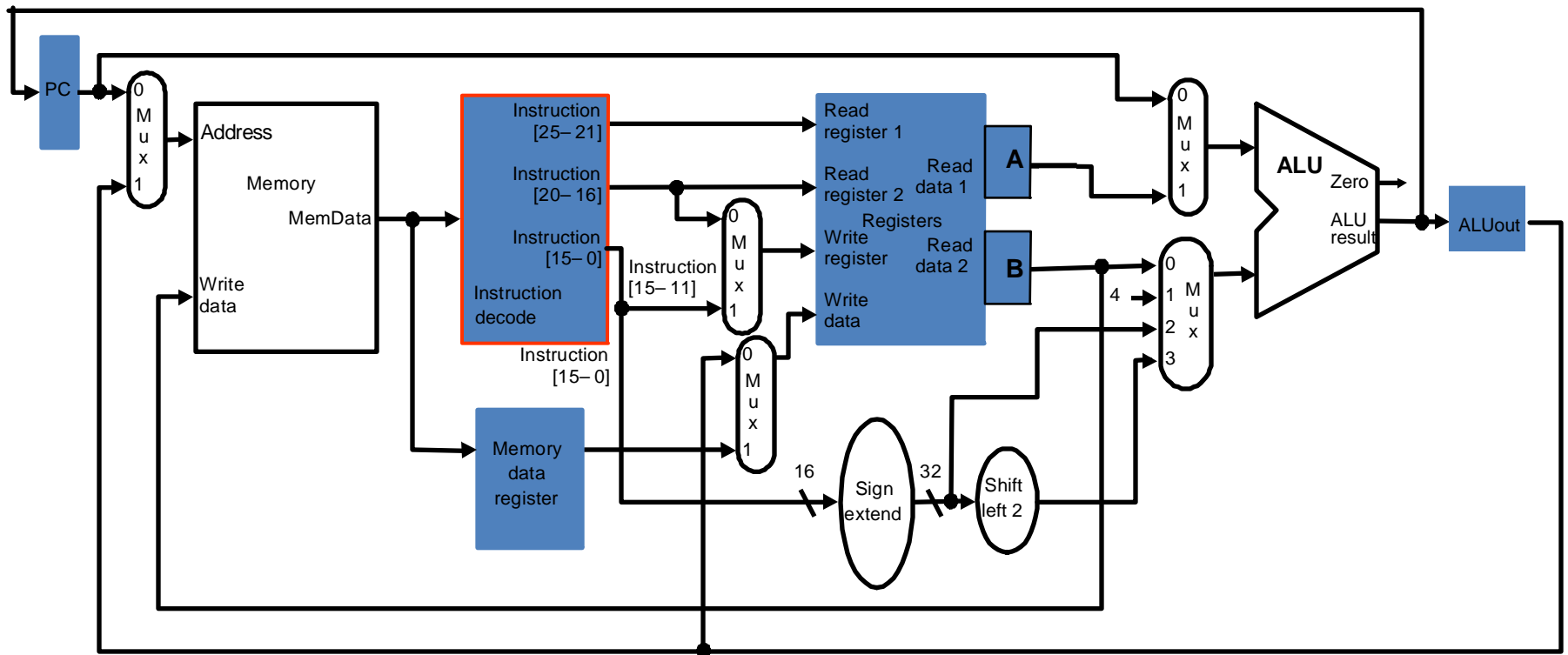- Instruction register is combined with instruction decode.




How does it work?

- R type instruction: $R[rd] \leftarrow R[rs] \text{ op } R[rt]$
- Five cycles:
 - Instruction fetch
 - Instruction decode, read $R[rs]$ and $R[rt]$
 - Execute instruction: $R[rs] \text{ op } R[rt]$
 - Write result back to register $R[rd]$
 - Update PC: $PC = PC + 4$


R type: 1st cycle

- Instruction fetch

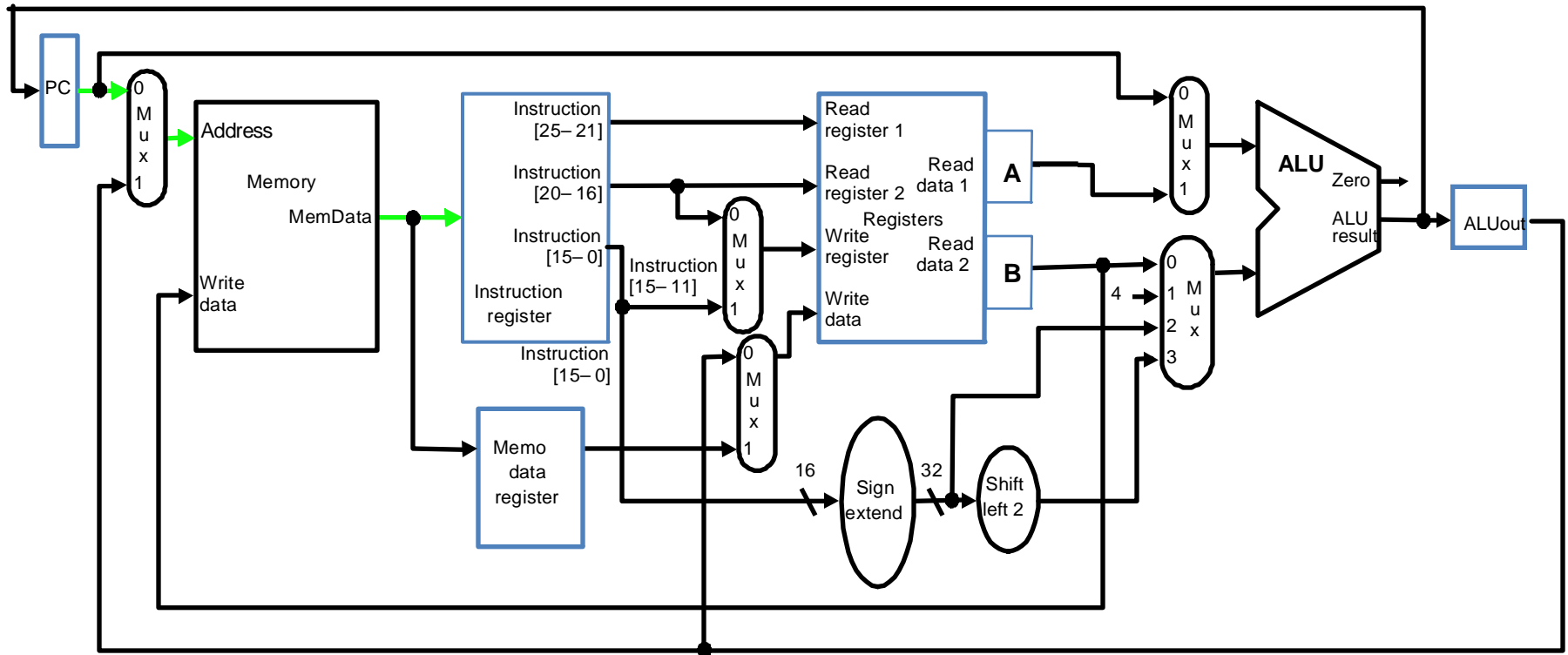


R type: 2nd cycle

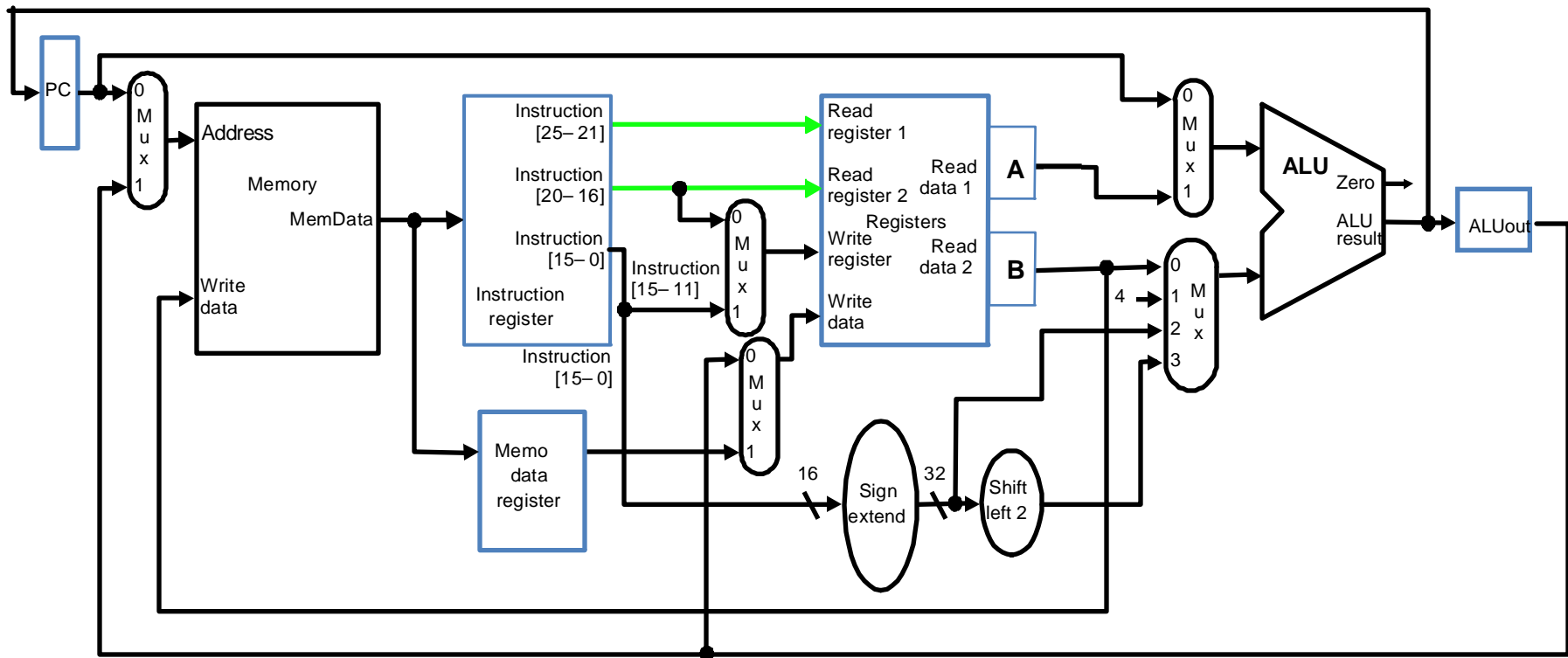- Instruction decode: read R[rs] and R[rt]




R type: 3rd cycle

- Execute instruction

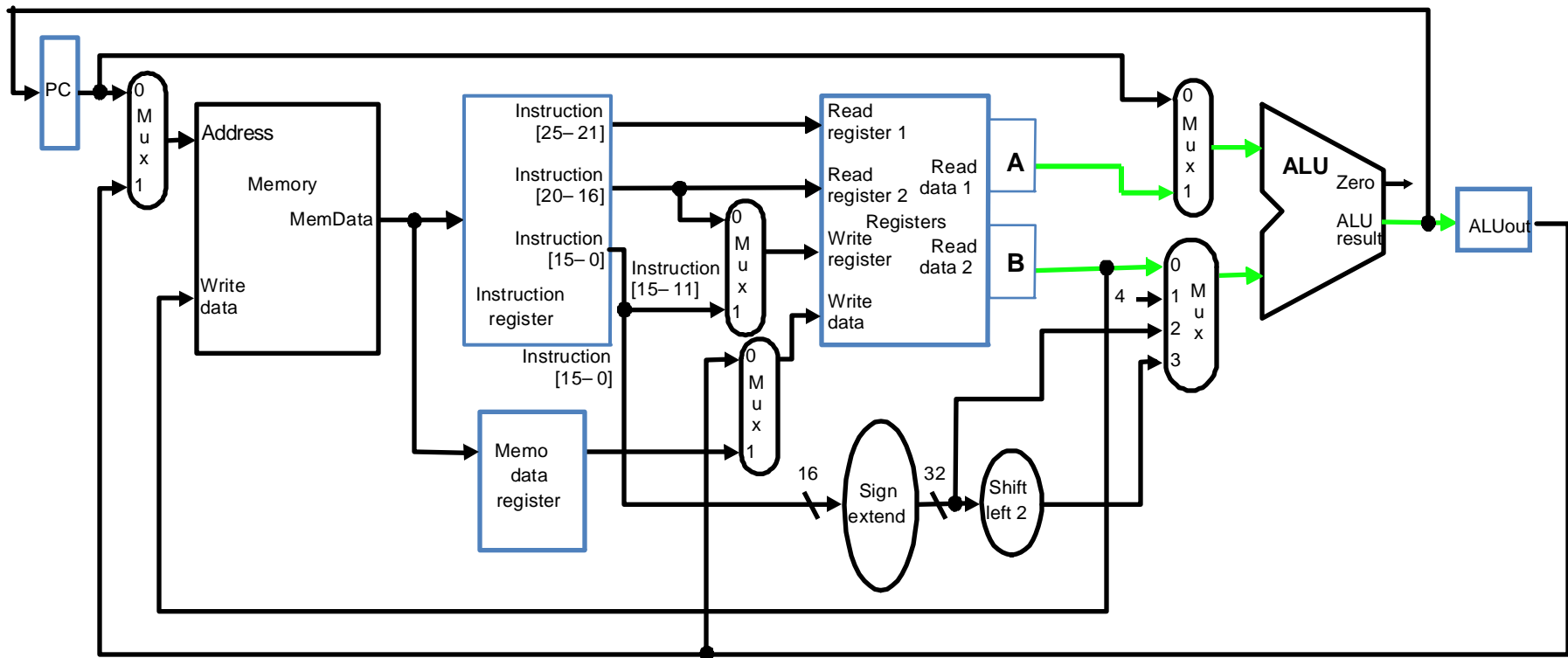


R type: 4th cycle

- Write result back to register R[rd]

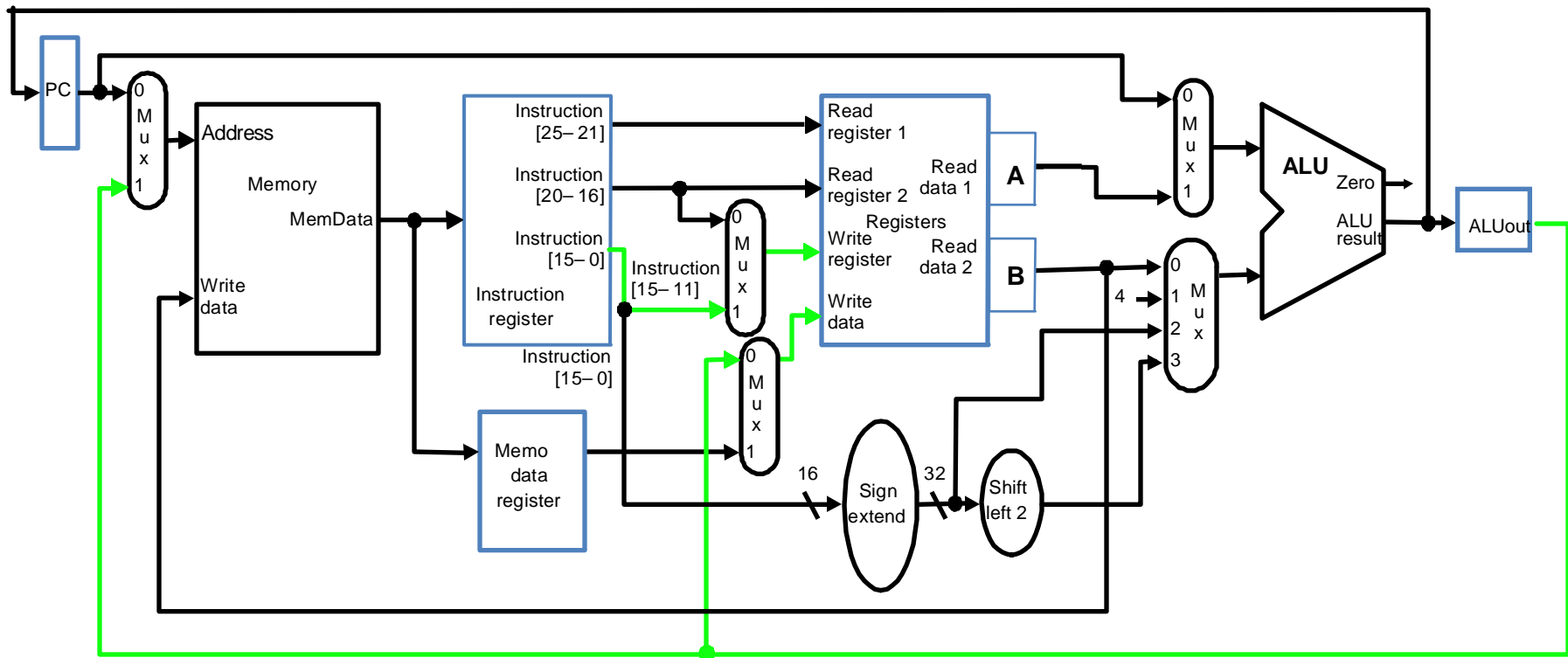

R type: 5th cycle

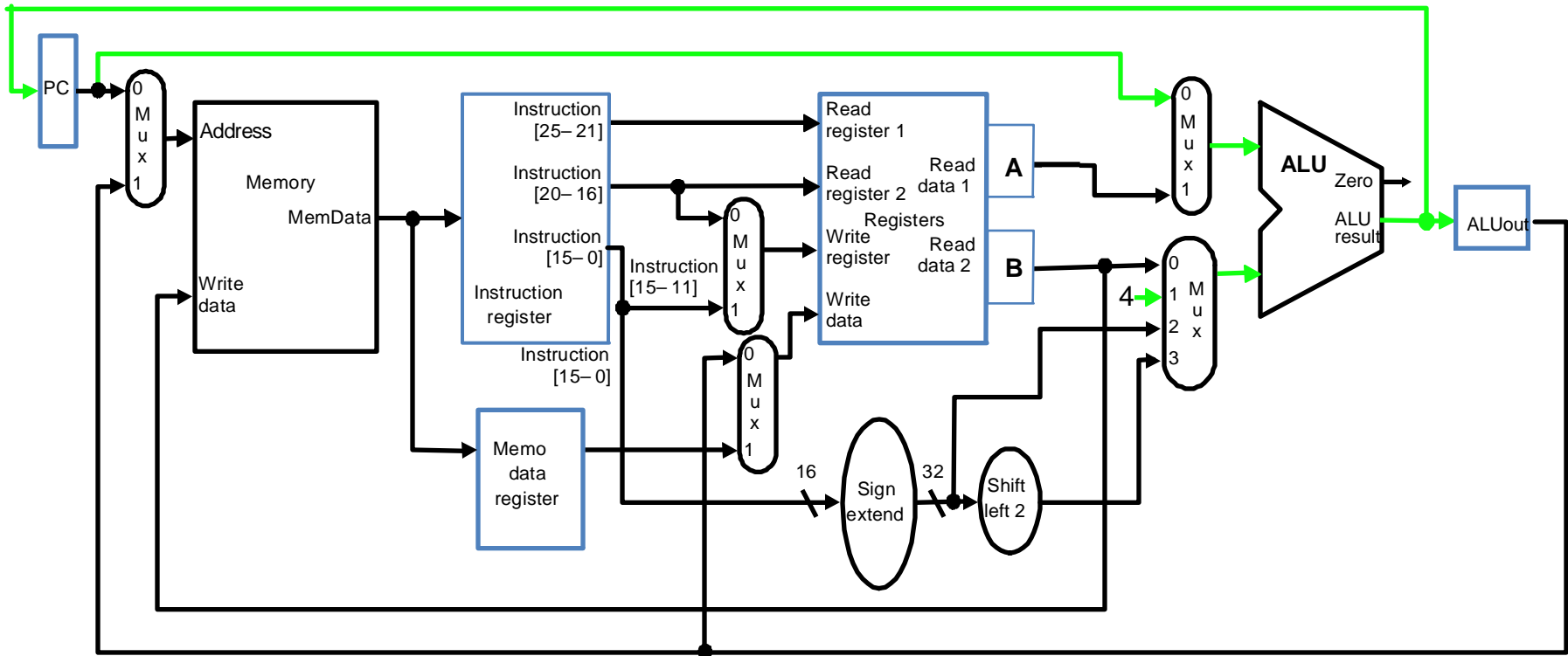- Update program counter: $PC = PC + 4$
- Instruction at $(PC + 4)$ will be fetched next time




How does it work?

- I type instruction: $R[rt] \leftarrow R[rs] \text{ op Imm}$
- Five cycles:
 - Instruction fetch
 - Instruction decode, read $R[rs]$
 - Execute instruction: $R[rs] \text{ op Imm}$
 - Write result back to register $R[rt]$
 - Update PC: $PC = PC + 4$


I type: 1st cycle

- Instruction fetch

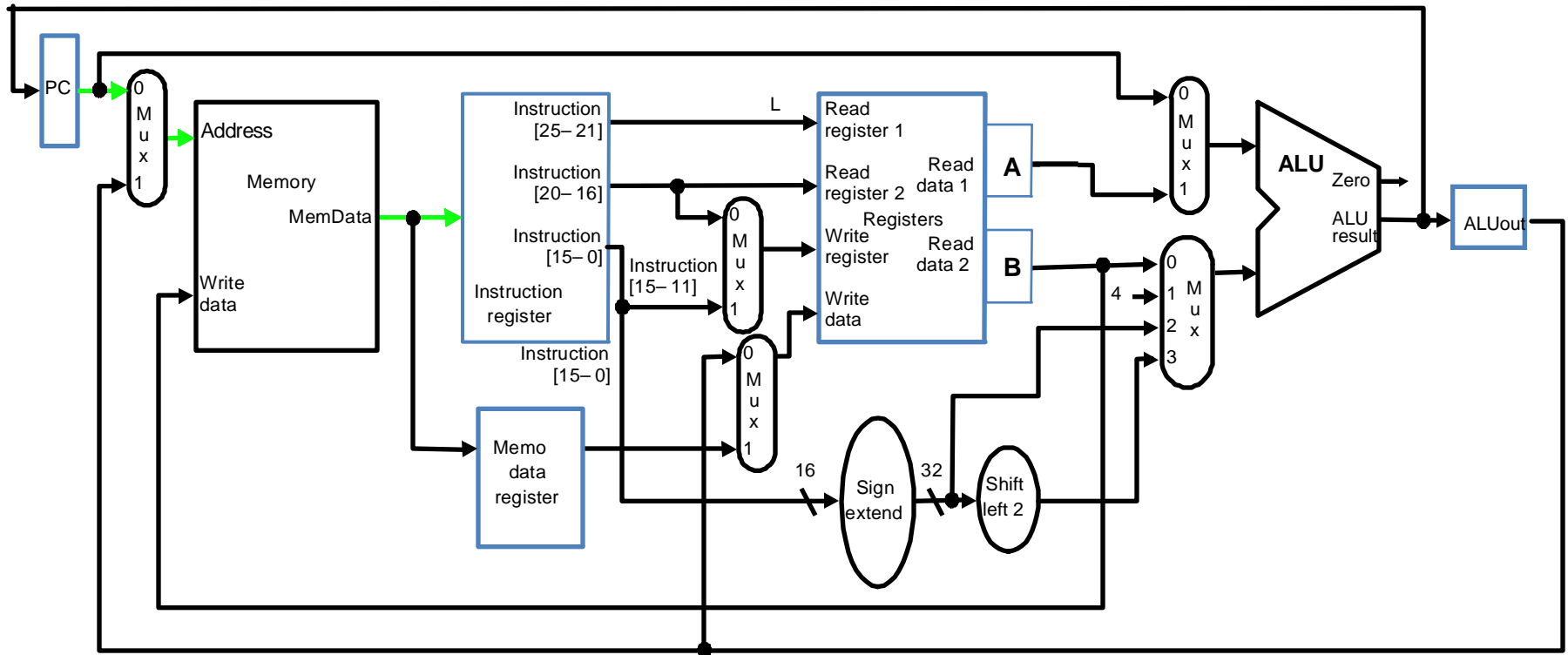


I type: 2nd cycle

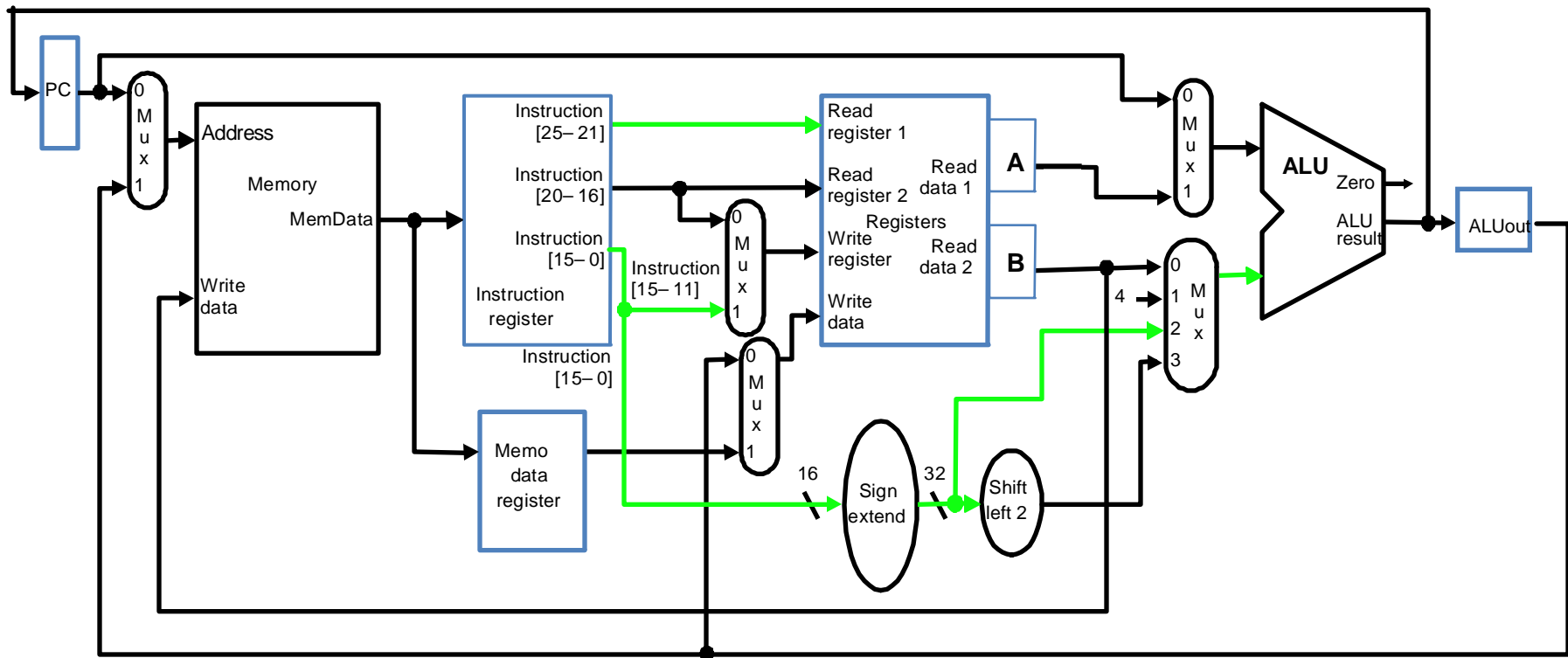- Instruction decode: read R[rs], decode Imm




I type: 3rd cycle

- Execute instruction: R[rs] op Imm

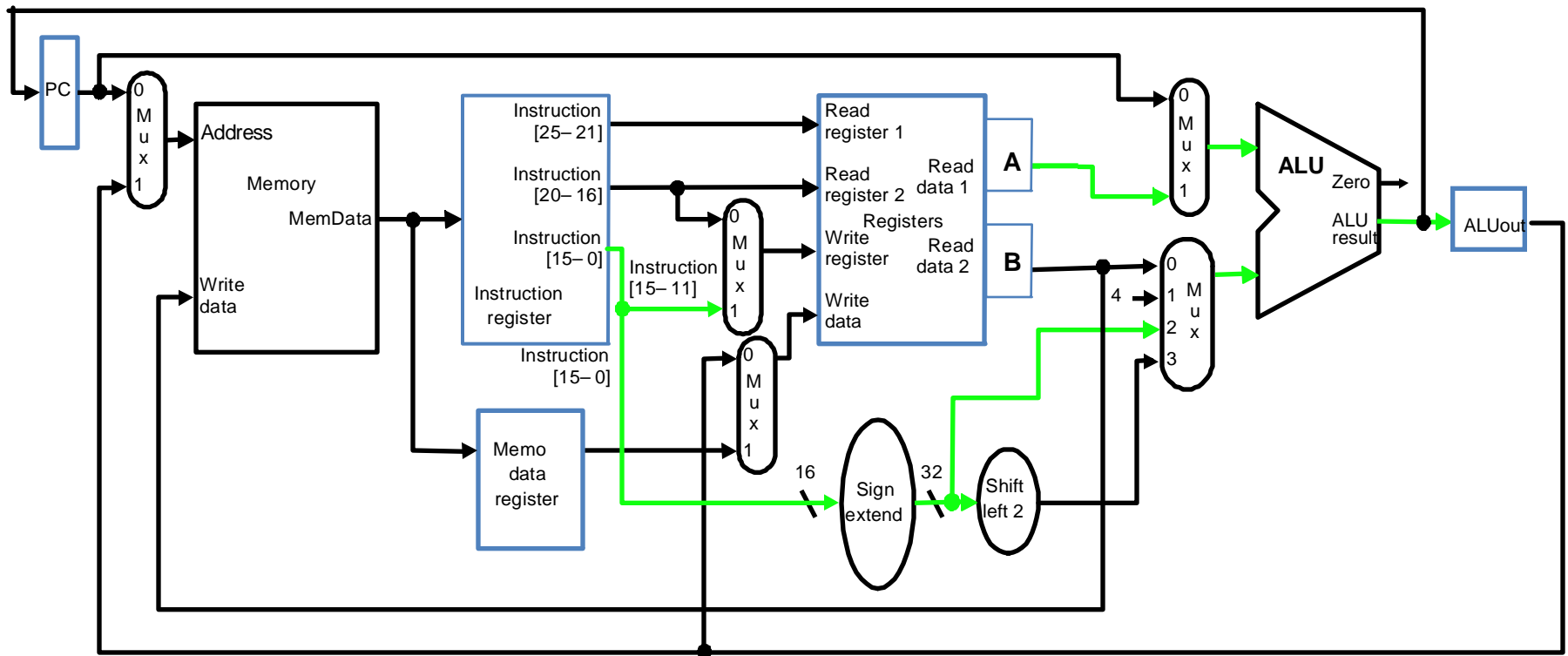


I type: 4th cycle

- Write result back to register R[rt]

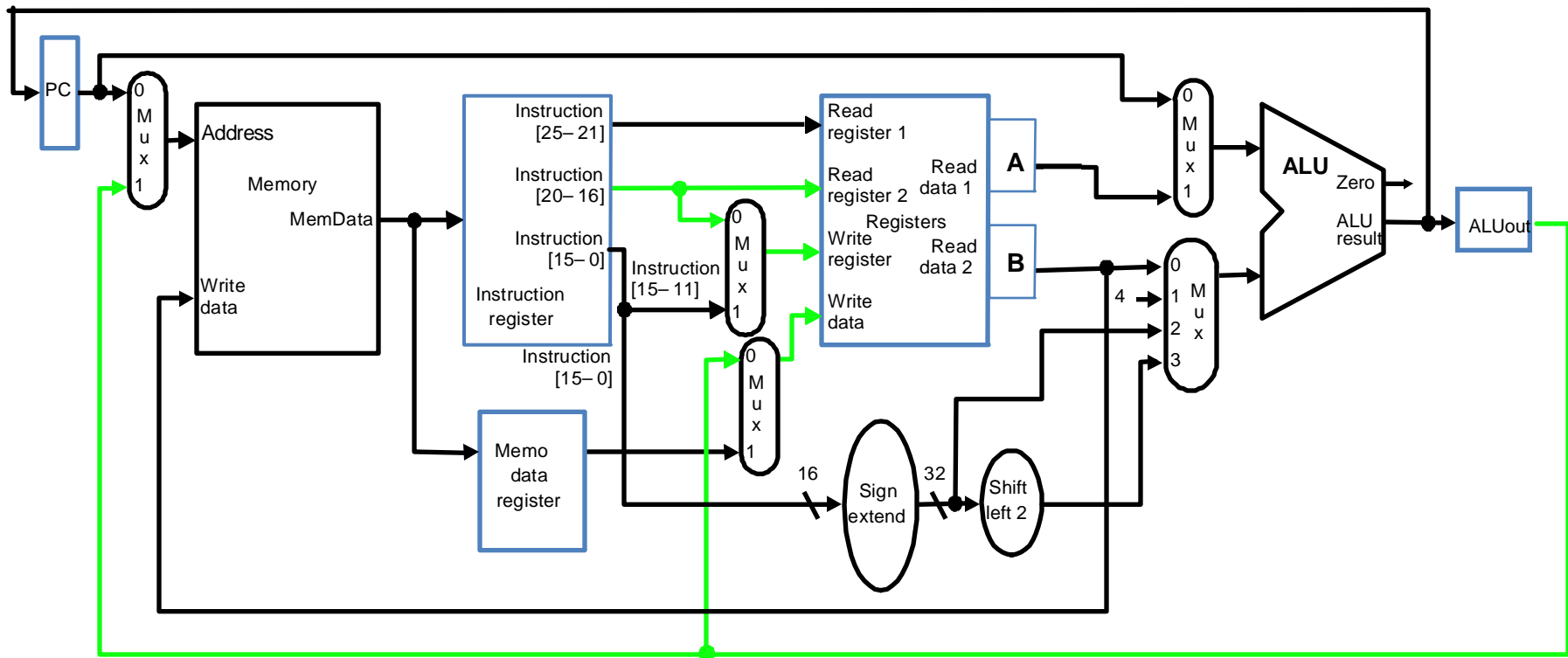

I type: 5th cycle

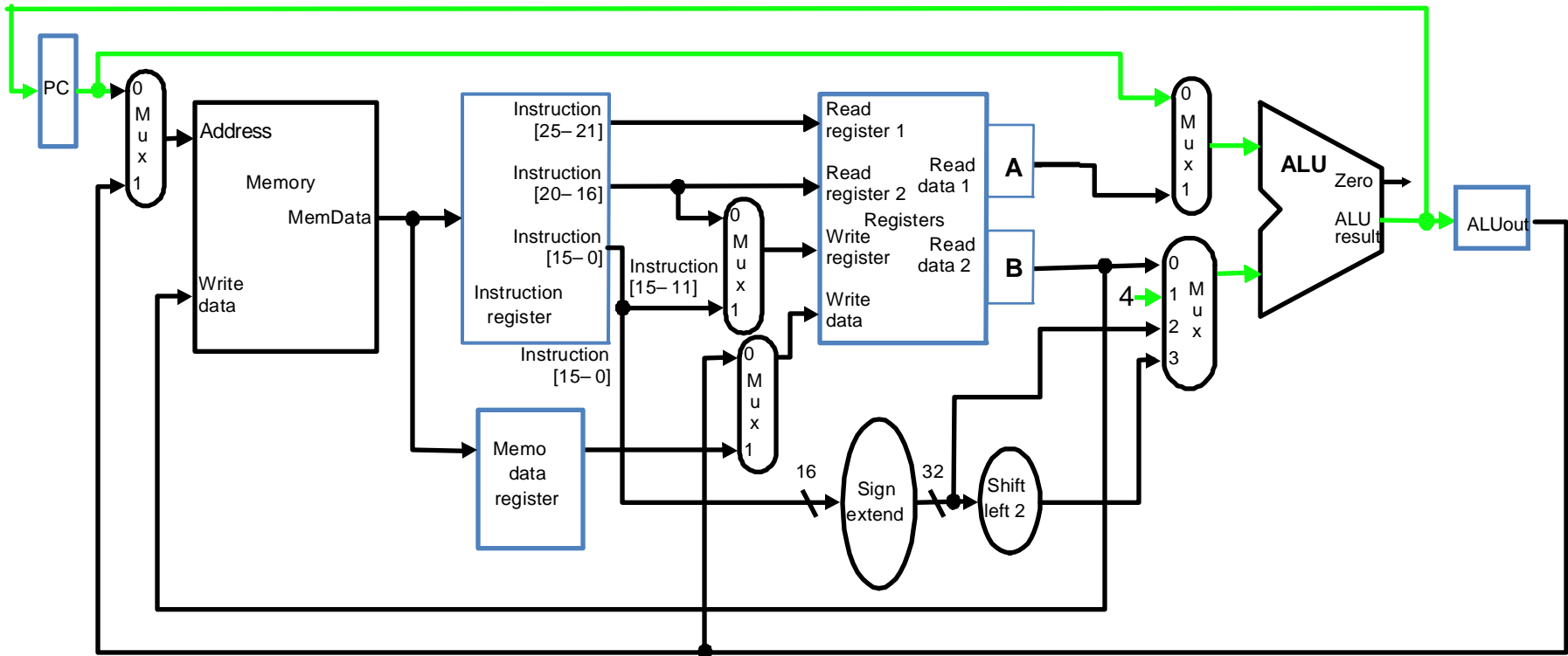- Update program counter: $PC = PC + 4$
- Instruction at $(PC + 4)$ will be fetched next time




How does it work?


- Load word: lw R[rt], Imm[R[rs]]
- Major cycles:
 - Instruction fetch
 - Instruction decode: read R[rs]
 - Calculate memory address: $R[rs] + Imm$
 - Load data from memory address: $R[rs] + Imm$
 - Write memory data to register R[rt]
 - Update PC: $PC = PC + 4$

Calculate memory address

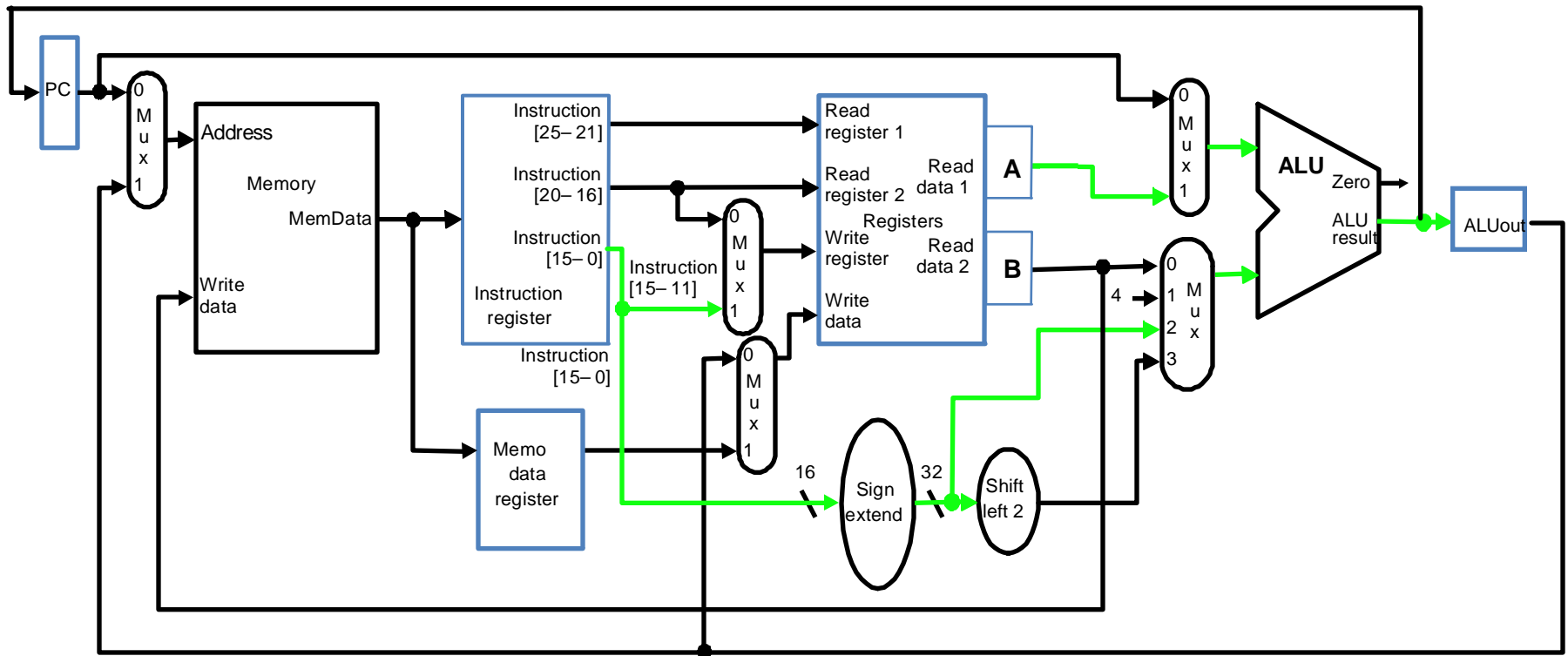
- $\text{address} = R[\text{rs}] + \text{Imm}$



Load data from memory

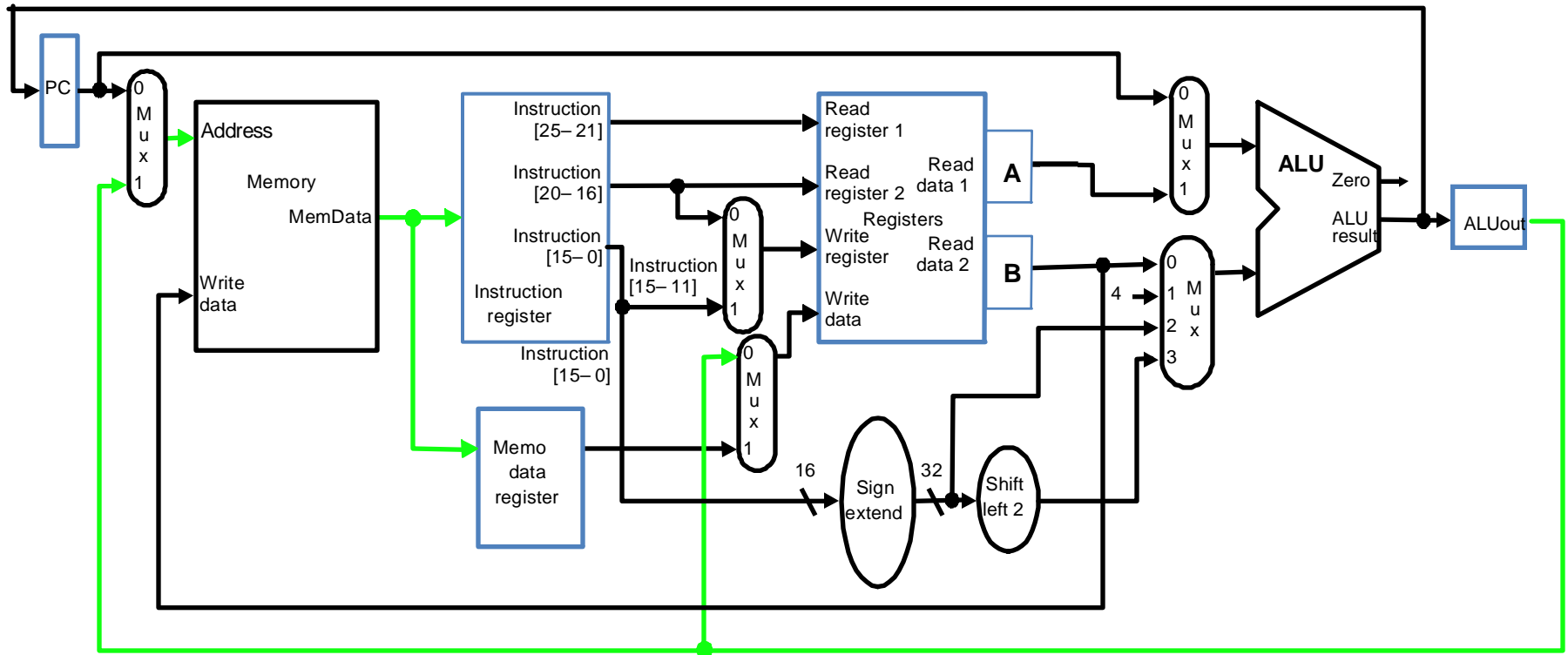

Write memory data to R[rt]

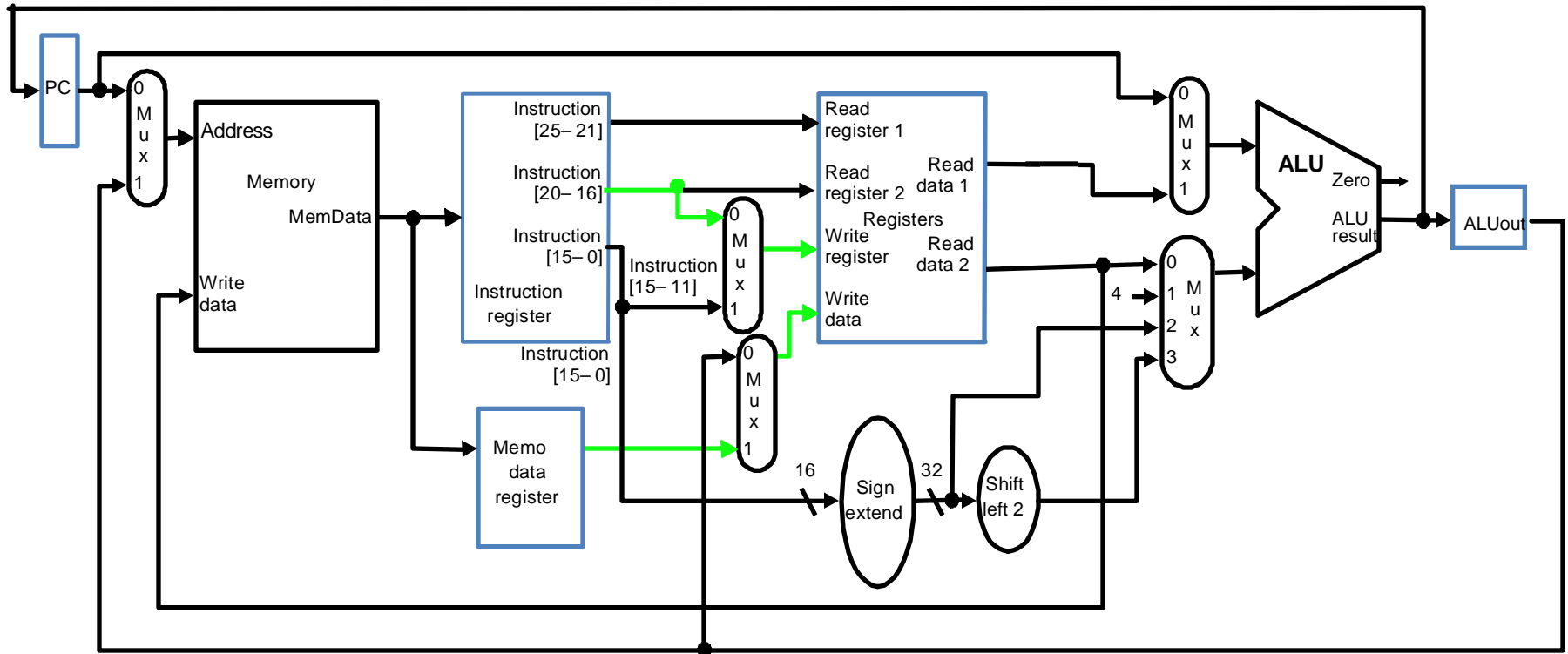


How does it work?


- Store word: `sw R[rt], Imm[R[rs]]`
- Major cycles:
 - Instruction fetch
 - Instruction decode: read `R[rs]`
 - Calculate memory address: `R[rs] + Imm`
 - Store data from `R[rt]` to memory
 - Update PC: `PC = PC + 4`

Calculate memory address

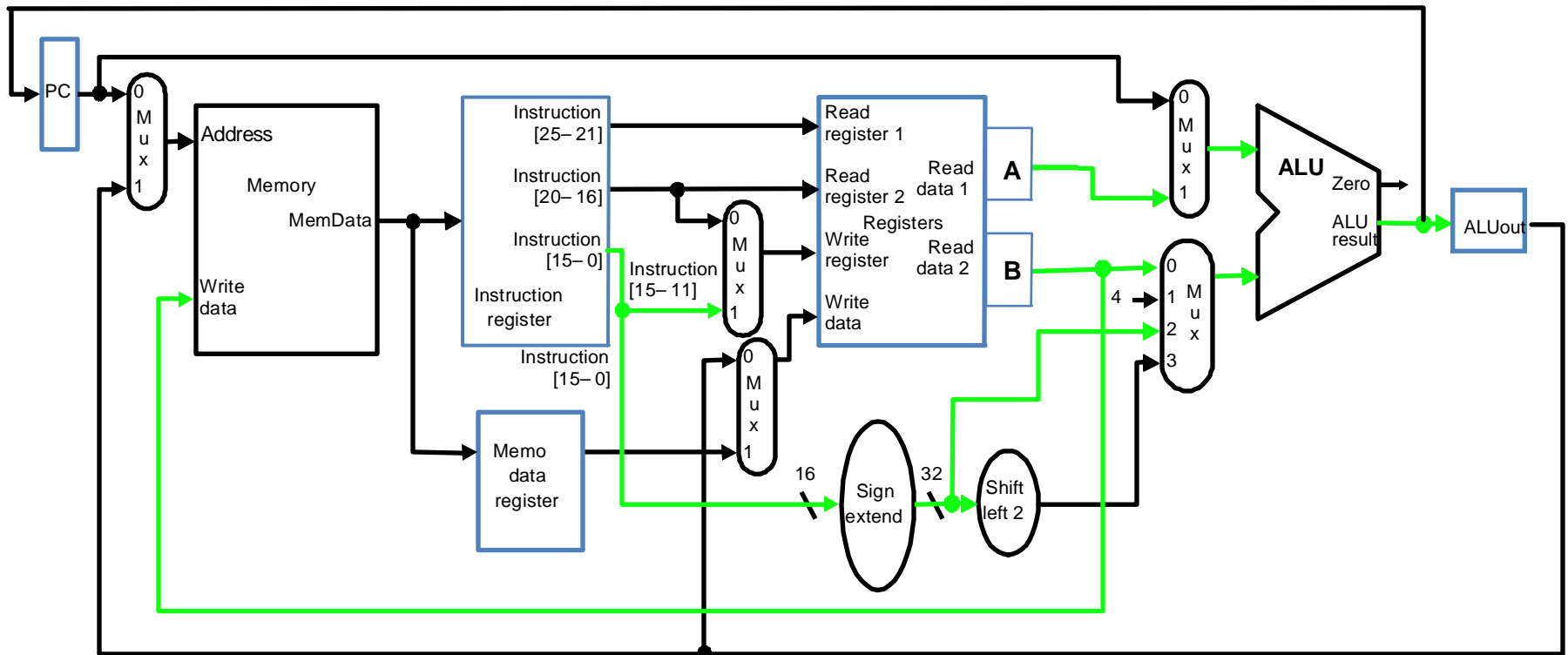- $\text{address} = R[\text{rs}] + \text{Imm}$
- ALUout is used to store the calculated address which will be used in the store stage later.
- Read $R[\text{rt}]$




Store data from register to memory

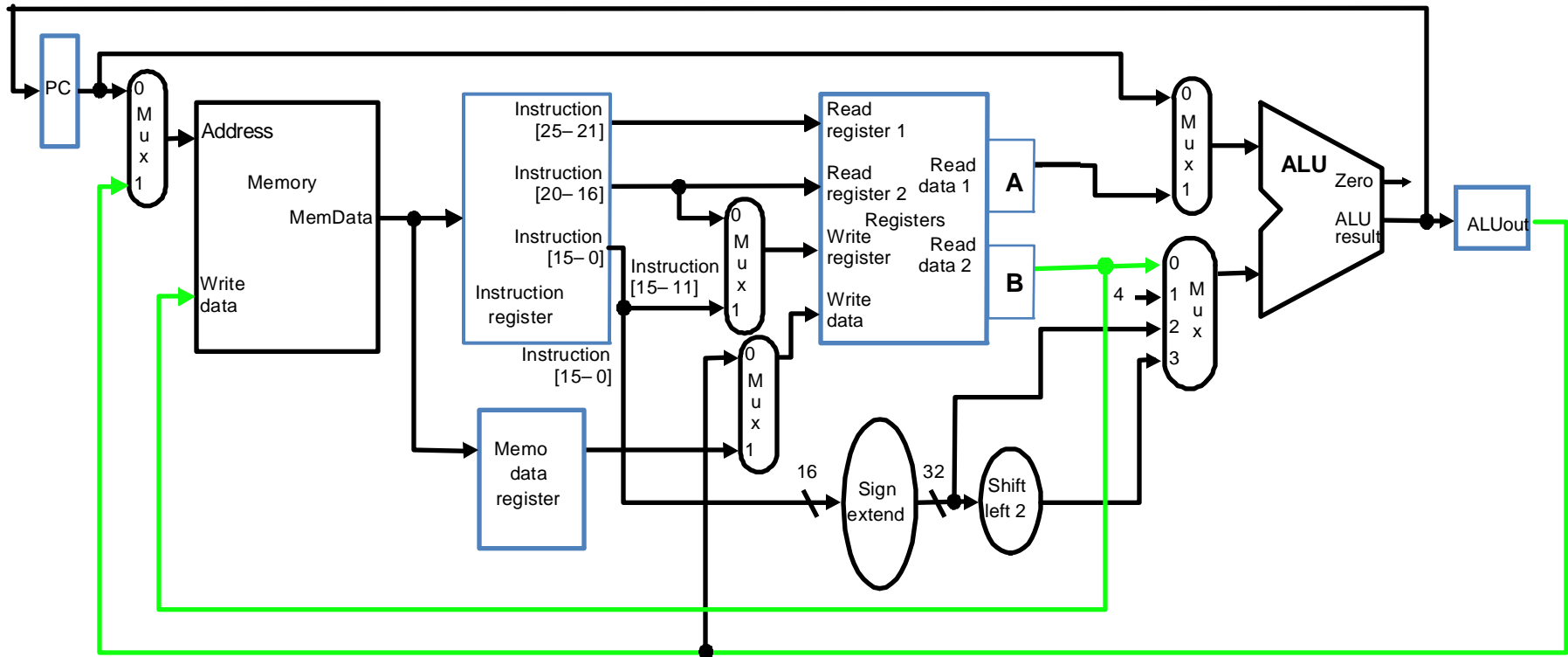

How does it work?


- Branch instruction: beq R[rt], R[rs], Imm
- Three major cycles
 - Instruction fetch
 - Instruction decode: read R[rs] and R[rt]
 - Calculate $(PC + 4)$
 - Calculate $(PC + 4 + Imm \times 4)$
 - Calculate branch condition: e.g. $R[rt] == R[rs] ??$
 - Update program counter as $(PC + 4 + Imm \times 4)$ if branch condition is true

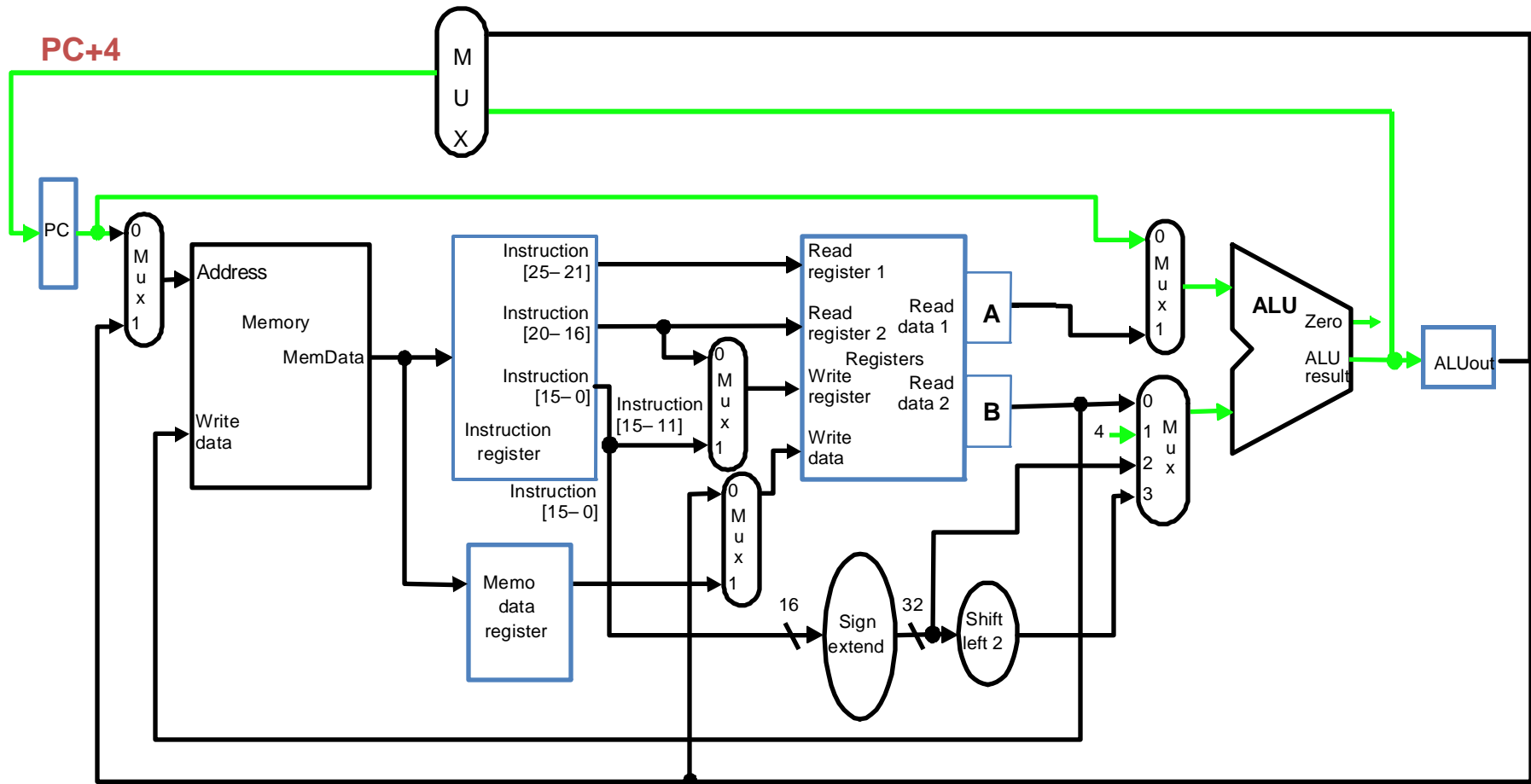- Add a multiplexer
- Calculate $PC + 4$, and write $(PC+4)$ to register PC



Calculate branch address

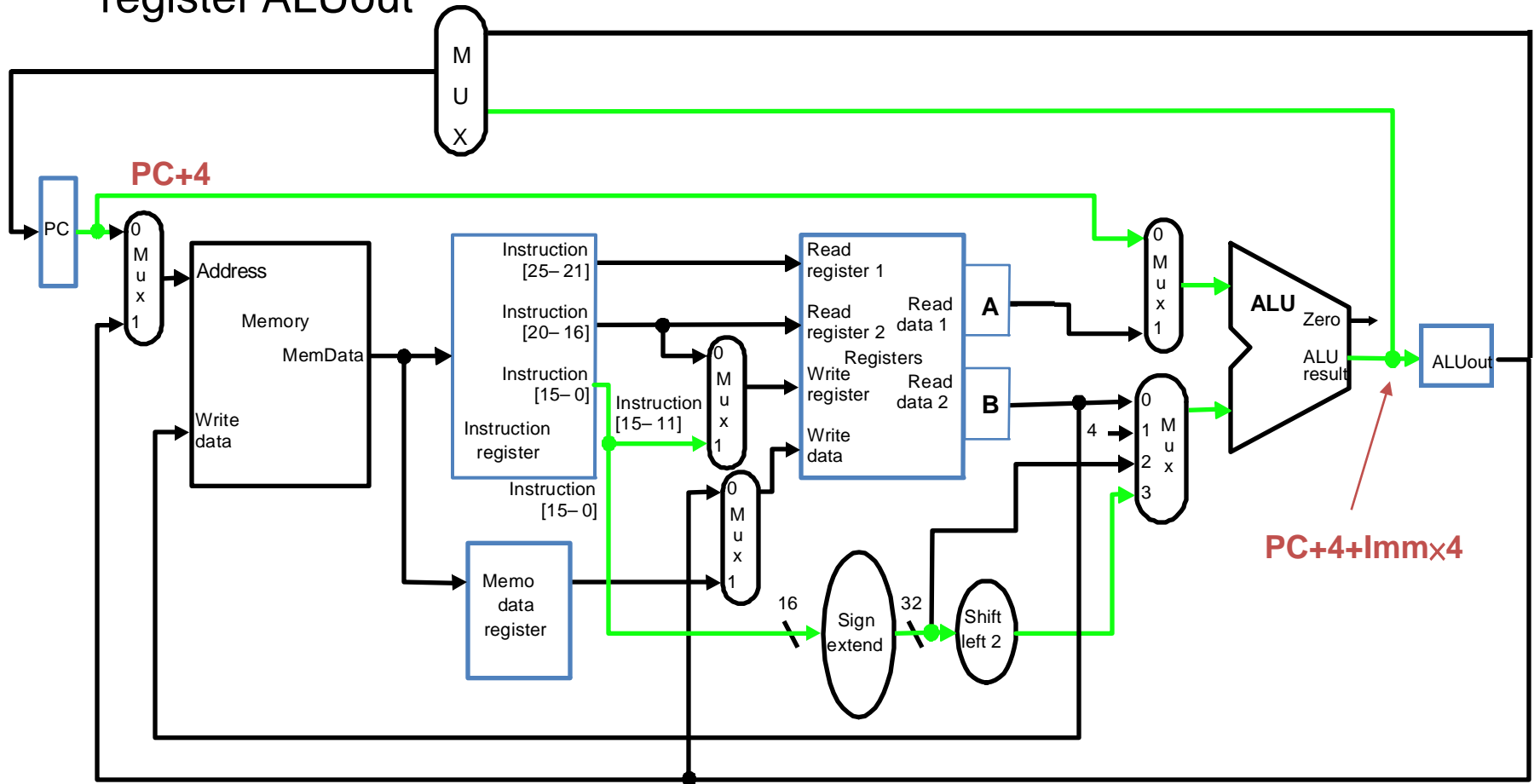- Branch address = $PC + 4 + Imm \times 4$
- Don't write branch address to register PC, write branch address to register ALUout




Calculate branch condition

- Calculate $R[rs] - R[rt]$
- Update register PC based on zero flag

Update PC if zero==1.
Otherwise, PC remains unchanged.

Select $(PC+4+Imm \times 4)$ if zero==1.

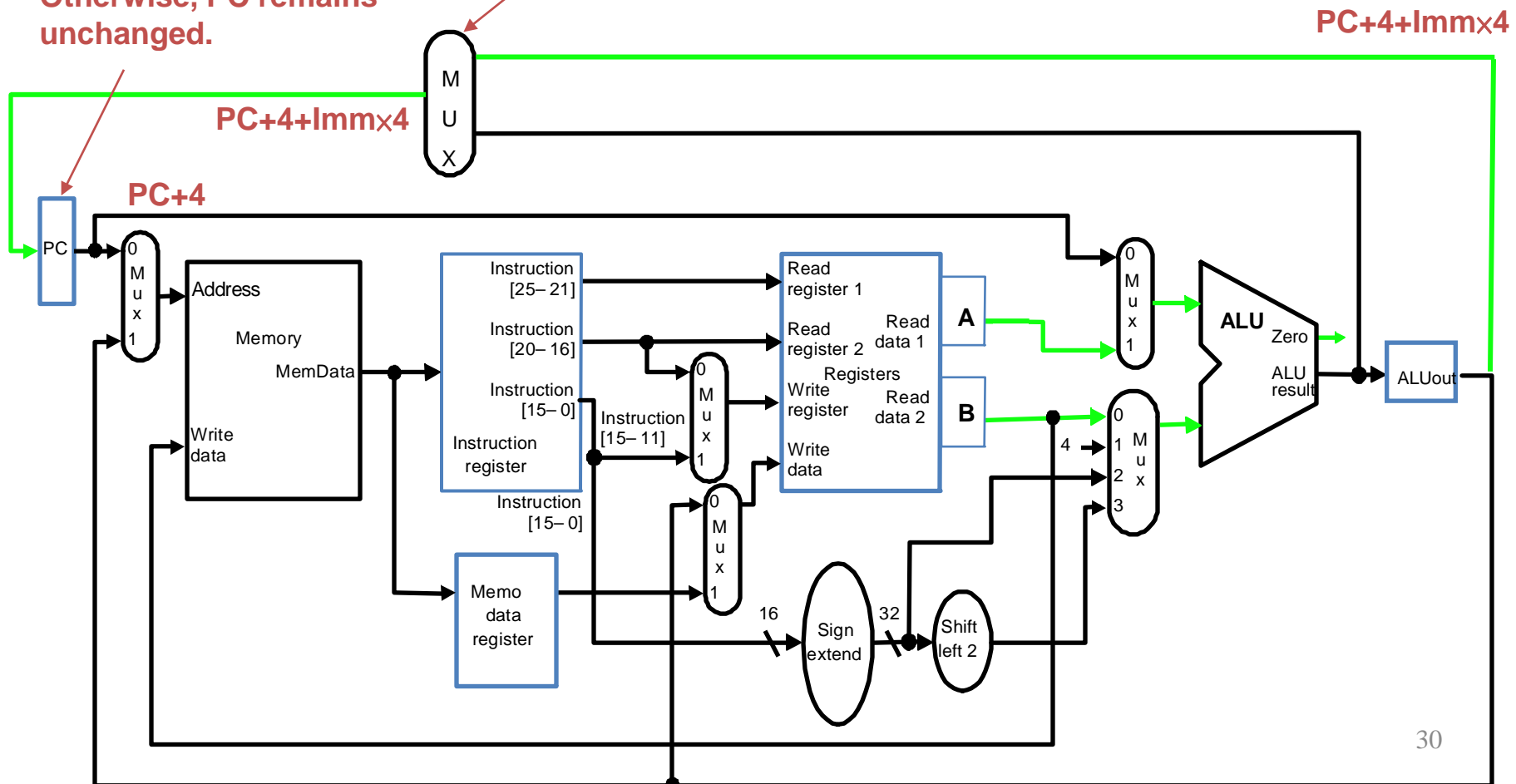


How does it work?

- Jump instruction: J Label
- One major cycle
 - Instruction fetch
 - Instruction decode
 - Calculate target address (2 steps)

Calculate (PC + 4)

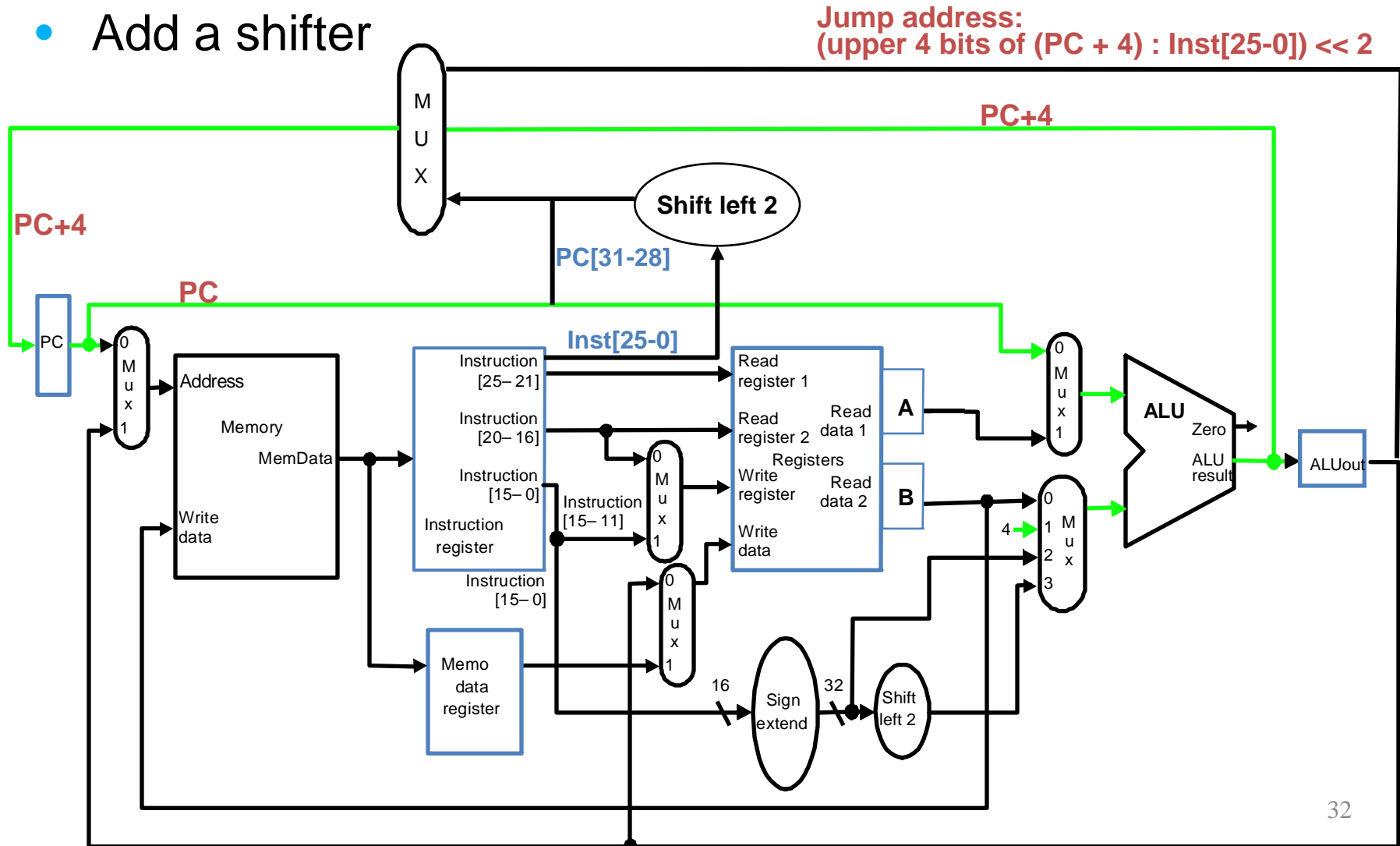
- Extend the multiplexer to 3 inputs
- Add a shifter



Calculate target address


- Calculate Jump address: (upper 4 bits of (PC + 4) : Inst[25-0]) << 2

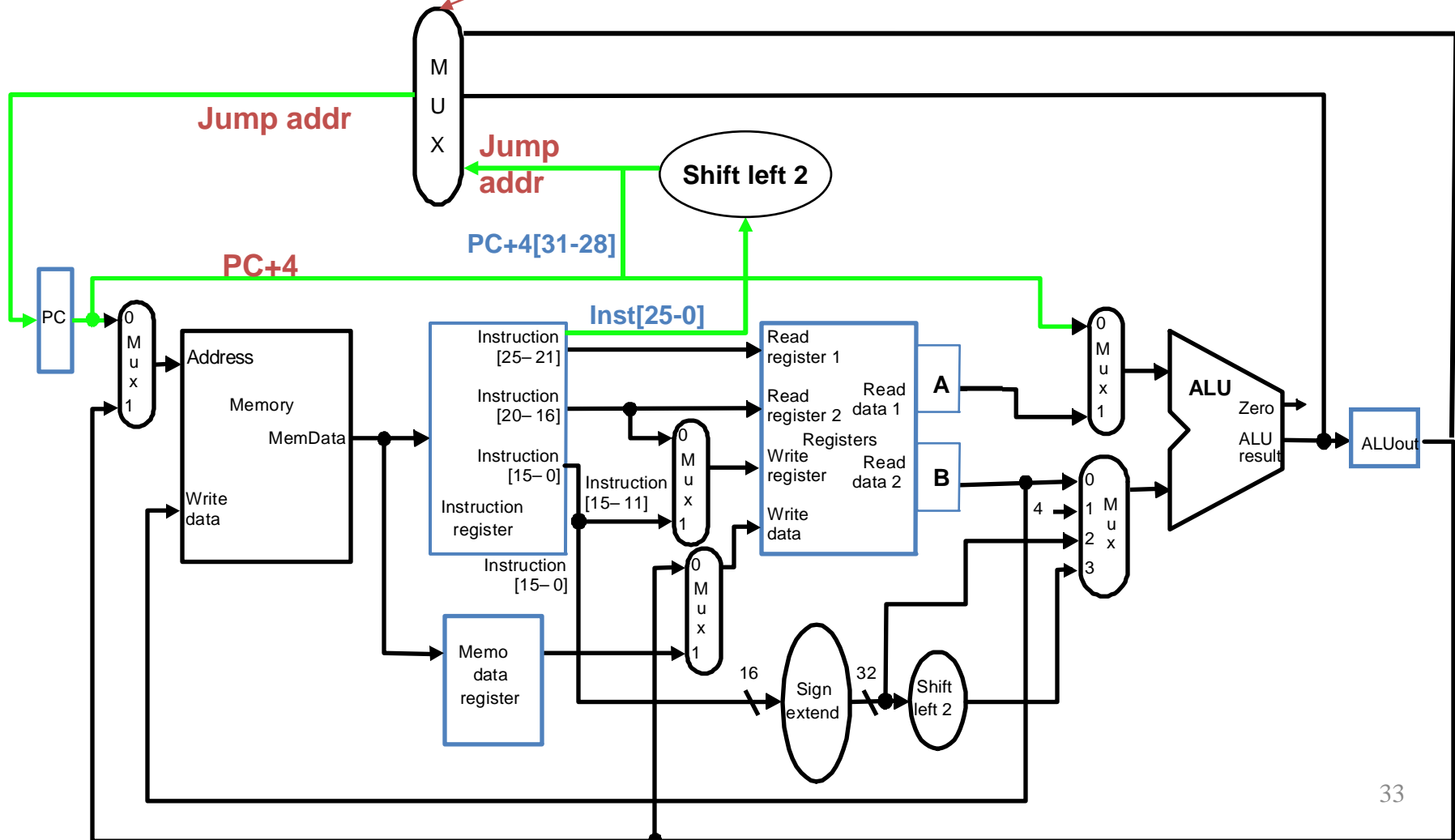Select jump address if it is jump instruction.



Multi-Cycle datapath with control signals

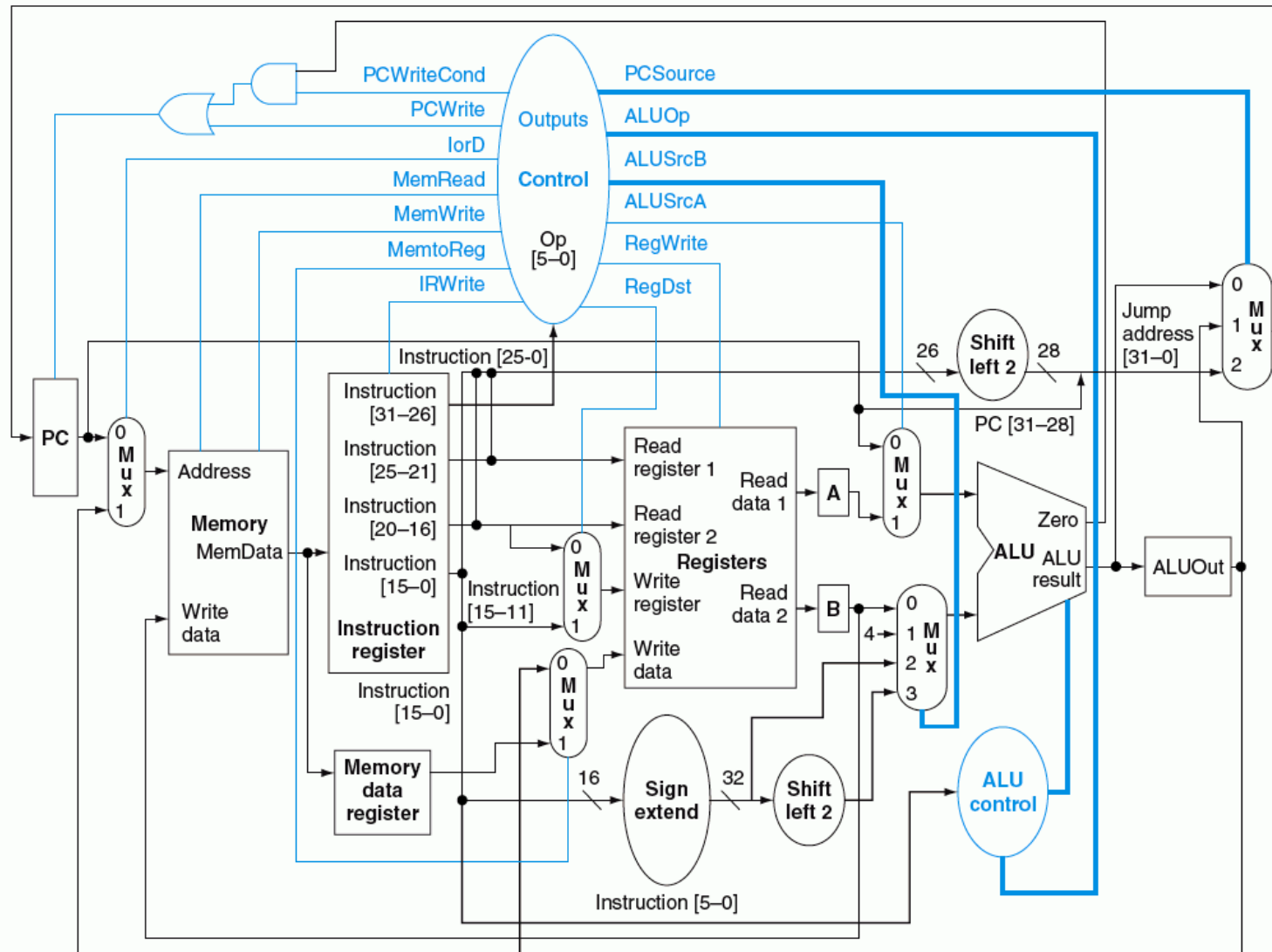
- Minimum Hardware: 1 memory, 1 ALU (instruction and data memories are combined, no adder to calculate branch address)



Designing control logic


Steps to execute instructions: R-type

- R-type, e.g. add \$t0, \$t1, \$t2
 - Instruction fetch
 - Instruction decode, read R[rs] and R[rt]
 - Execute instruction: R[rs] op R[rt]
 - Write result back to register R[rd]
 - Update PC: $PC = PC + 4$
- Can we design a finite state machine to represent these states? And generate different control signals at different states to control the operation of the datapath?
- E.g. design a FSM with 5 states: IF, ID, EX, WB, PC. Each state outputs appropriate control signals to control the datapath to finish adequate operation in a certain state.

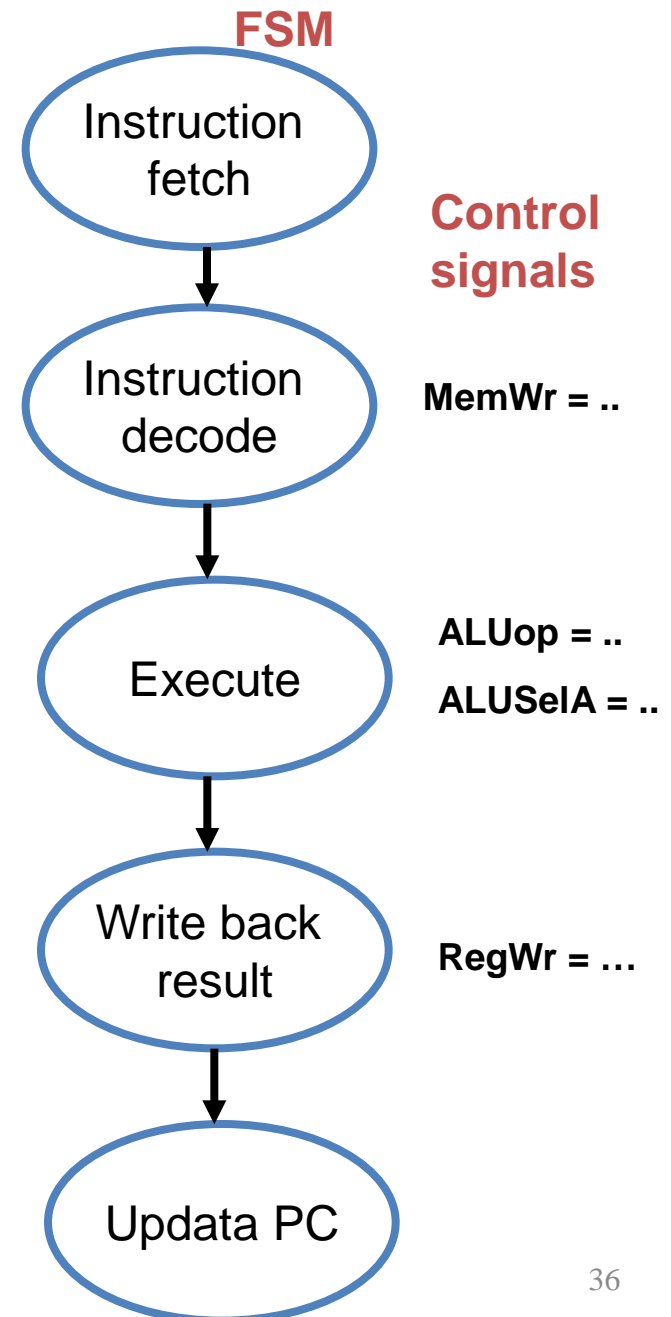

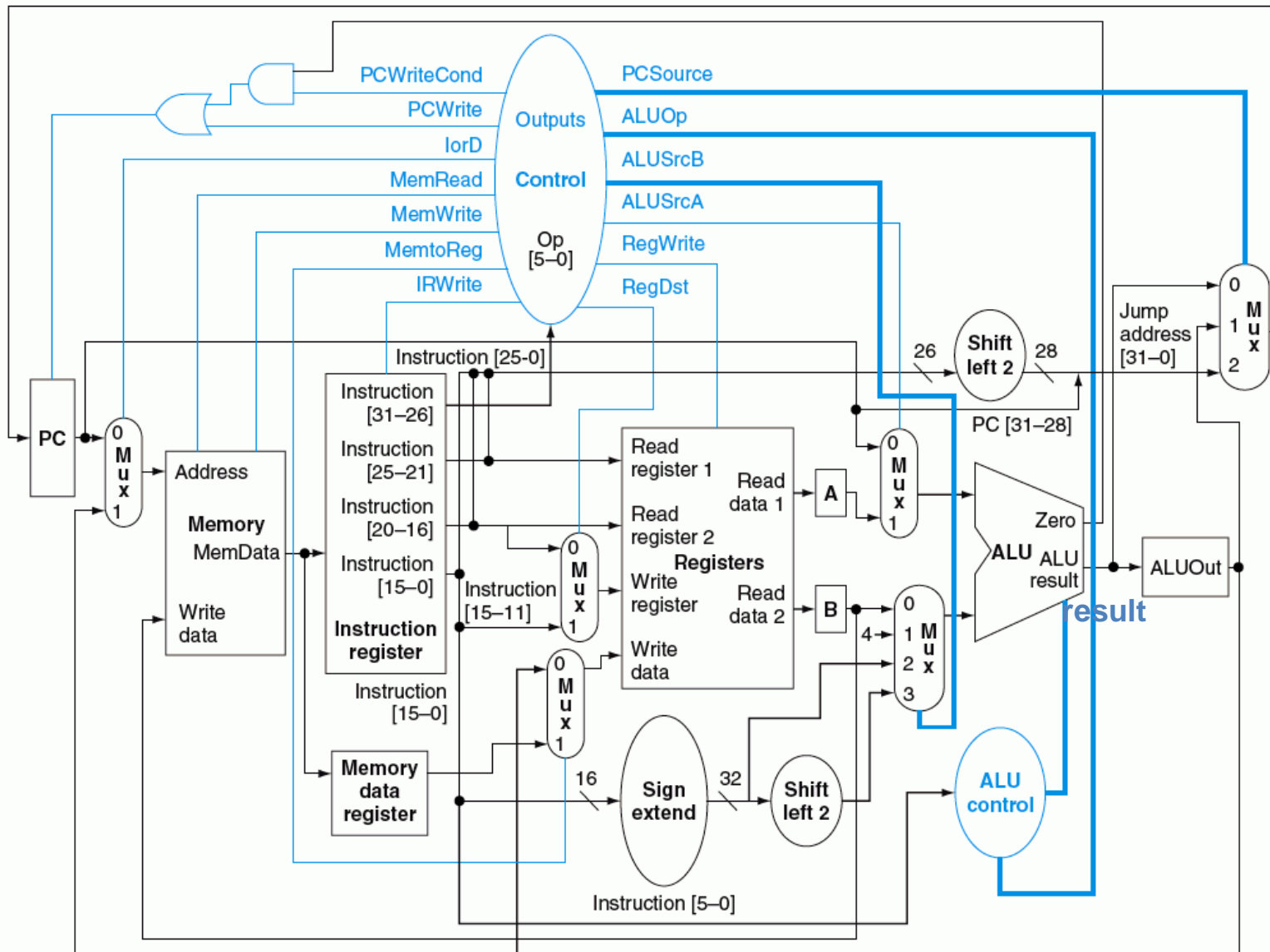
Example: control signals for $(\$t1 + \$t2)$ at execute state

- ALUOp = add, ALUSrcA = 1, ALUSrcB = 0, MemtoReg = x, **RegWrite = 0**



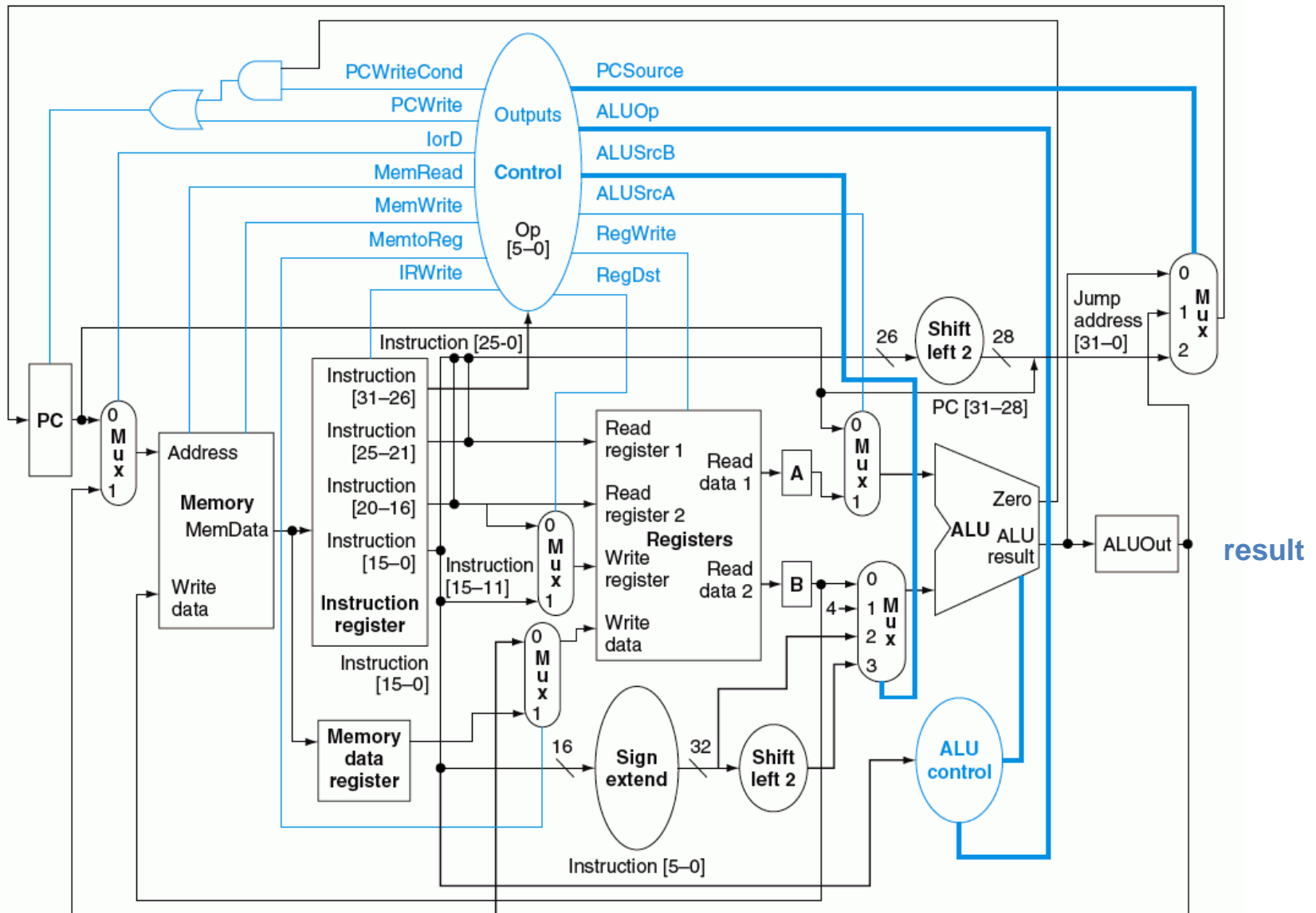
Example: control signals for (\$t1 + \$t2) at write back state

- ALUOp = x, ALUSrcA = x, ALUSrcB = x, MemtoReg = 0, RegWrite = 1




Steps involved in instructions: LW

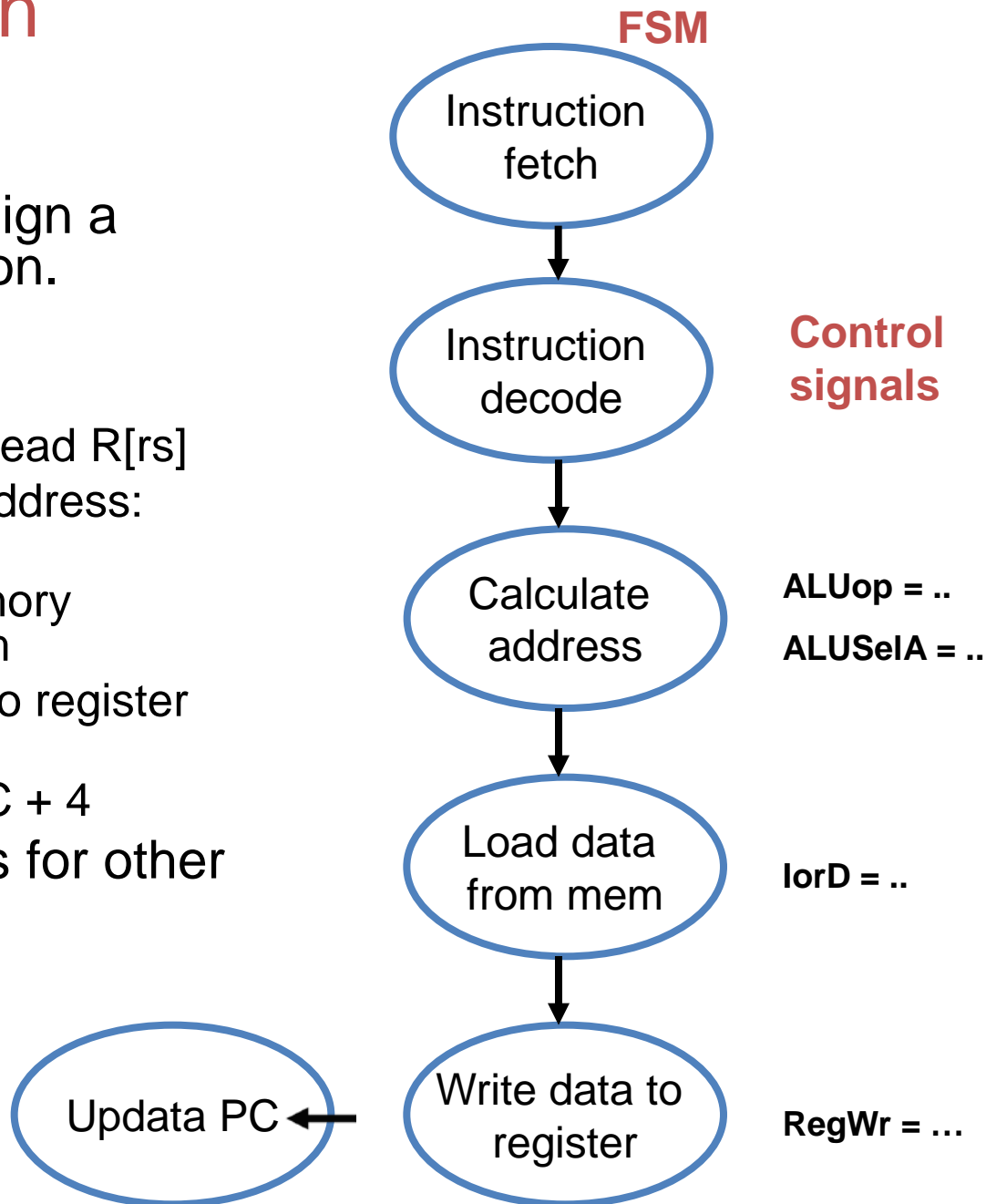- Similarly, we can design a FSM for LW instruction.
- Load word
 - Instruction fetch
 - Instruction decode: read $R[rs]$
 - Calculate memory address: $R[rs] + Imm$
 - Load data from memory address: $R[rs] + Imm$
 - Write memory data to register $R[rt]$
 - Update PC: $PC = PC + 4$
- We can design FSMs for other instructions.




Control FSM for the multi-cycle processor

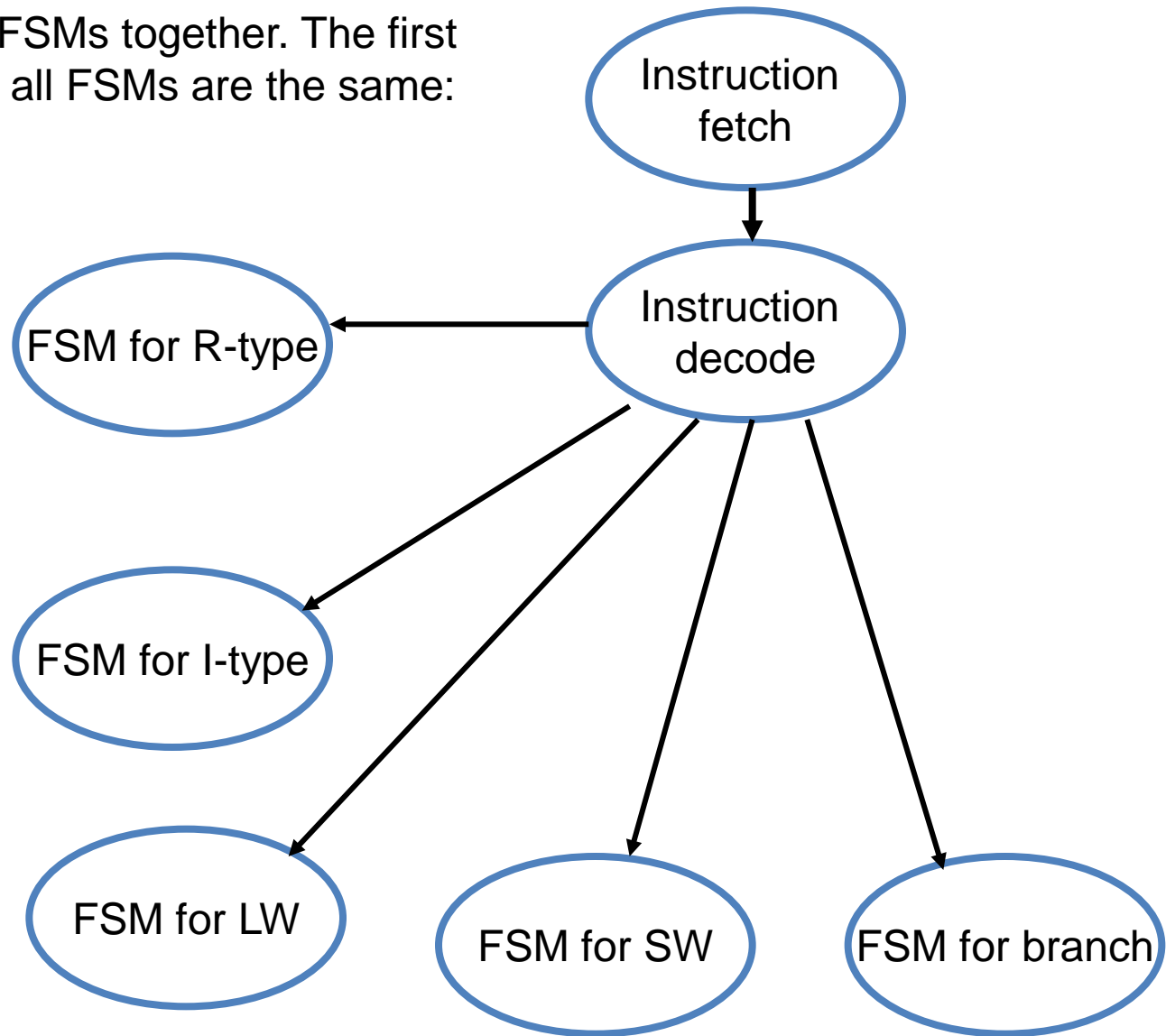- Combine all FSMs together. The first two states of all FSMs are the same: IF, ID.




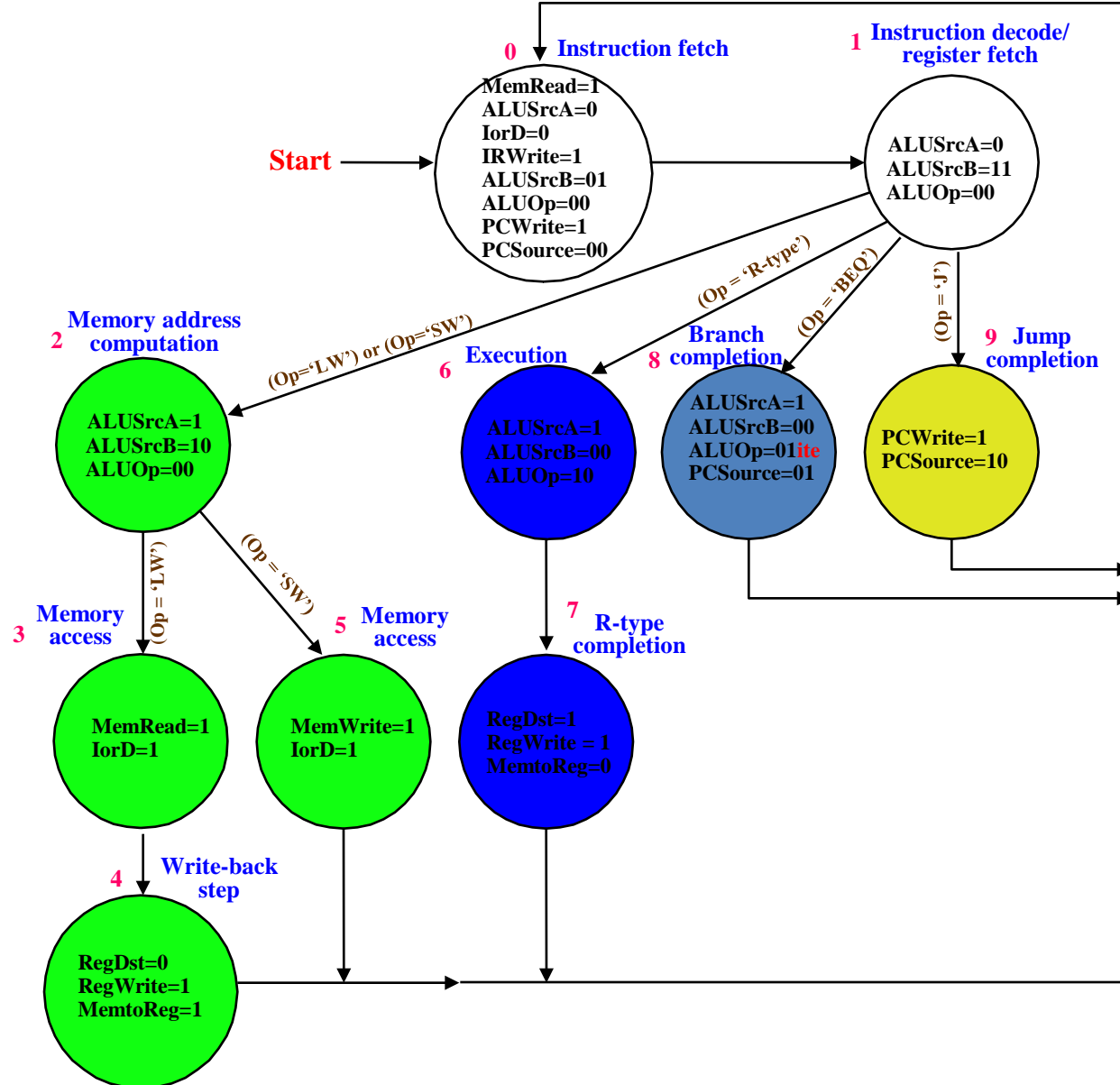Control FSM for the multi-cycle processor: a detailed view



Implement the FSM in hardware

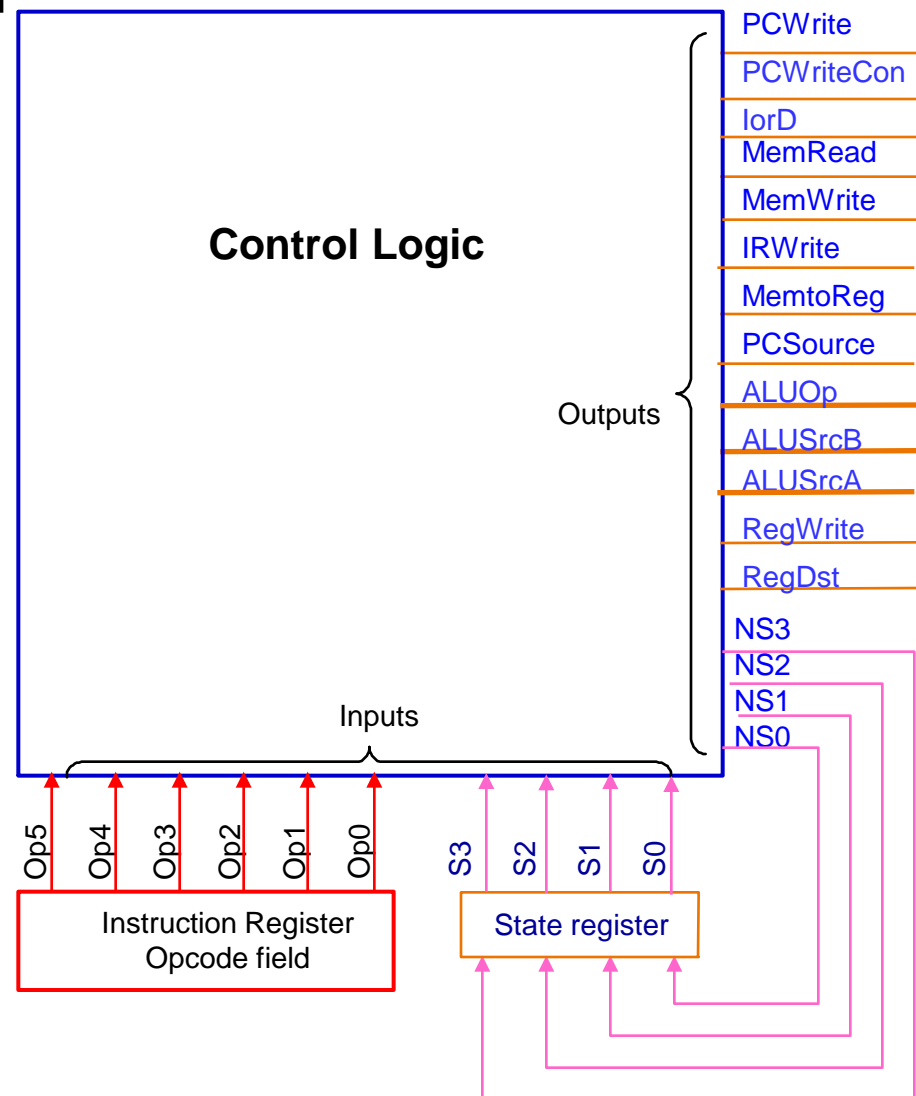- State changes depends on opcode and current state.



Single cycle vs Multi-cycle processor

- Example
 - A single cycle processor has a cycle time of 800ps
 - A multi-cycle processor: $CPI_{R\text{-type}}=4$, $CPI_{lw}=5$, $CPI_{beq}=3$. Cycle time = 200ps
 - A program has 40% R-type, 20% lw, 40% beq. Totally 10000 inst.
 - Single processor time = $10000 \times 800 \times 1 = 8M$ ps
 - Average CPI for multi-cycle processor = $4 \times 40\% + 5 \times 20\% + 3 \times 40\% = 3.8$
 - Multi-cycle processor time = $10000 \times 200 \times 3.8 = 7.6M$ ps
 - Multi-cycle processor is better in this example, how about 40% of lw, and 20% of beq?
 - $4 \times 40\% + 5 \times 40\% + 3 \times 20\% = 4.2$
 - $10000 \times 200 \times 4.2 = 8.4M$ ps
- Which processor is better?
 - Depends on the instruction mix of programs → program dependent.
 - Execution time = Instruction count \times CPI \times cycle time

Summary

- Two components of processors.
 - Datapath and control.
- Design multi-cycle processor.
 - Partition datapath of single cycle processor (break an instruction execution into multiple steps).
 - Add registers into the partitioned datapath.
 - Design FSM to control the datapath.
 - Execute each step in one cycle, require multiple cycles to execute one instruction.
- Advantages and disadvantages
 - Single cycle: $CPI = 1$, long cycle time.
 - Multi-cycle: shorter cycle time as each cycle just execute one step, different instructions have different CPI. As a result, simple instructions require less cycles (less time) to execute.
- Performance comparison
 - Program dependent.
 - Execution time = Instruction count \times CPI \times cycle time

